

Solutions

Short Answers

①

$$(d) i_s(t) = 3 \cos(40t + 50^\circ) A$$

same frequency (LTI ckt)

same phase (resistive ckt)

①


$$P_{\text{avg}} = \frac{1}{2} \operatorname{Re} \left\{ 5 e^{j50^\circ} \times 3 e^{-j50^\circ} \right\} = \frac{15}{2} = 7.5 W$$

①

(2)

$$i_s(t) = 5 \cos(30t)$$

$$\omega = 30 \text{ rad/s}$$

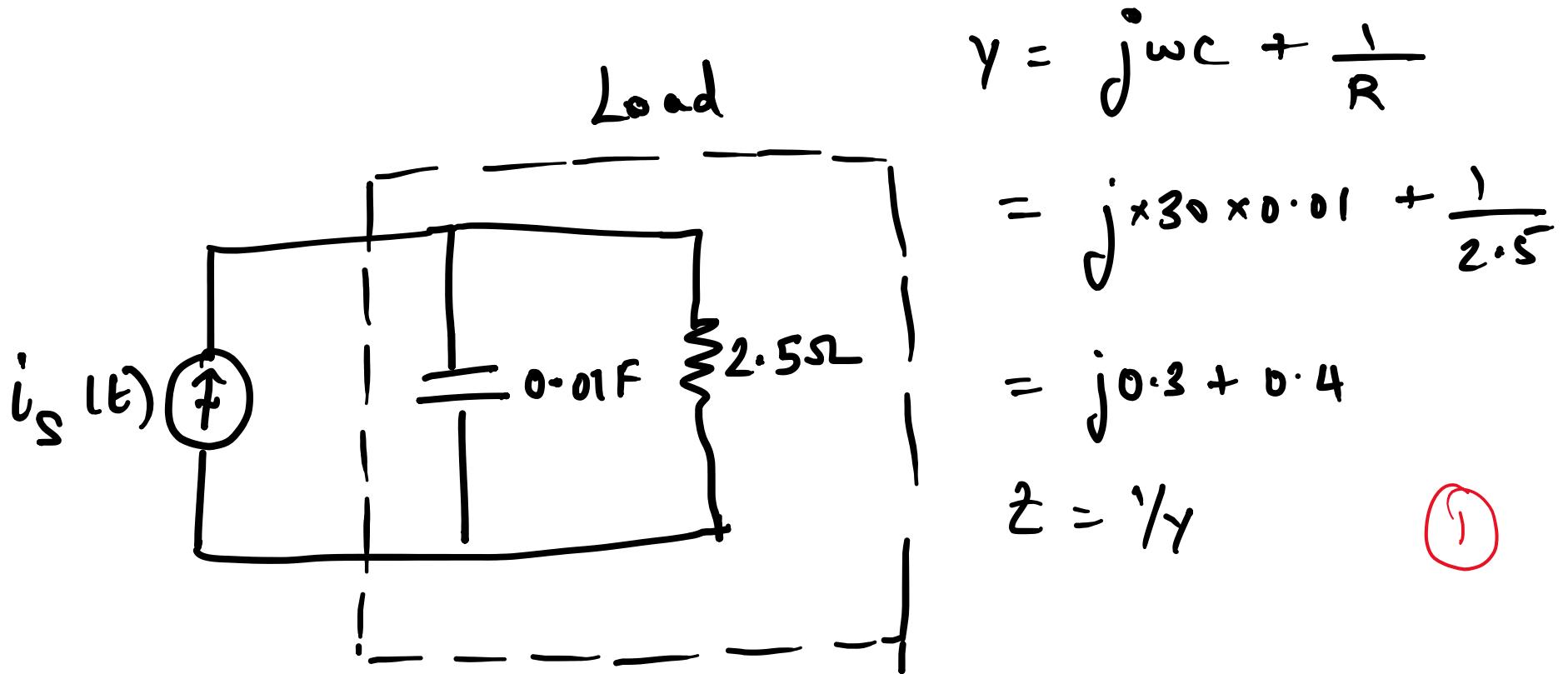

(1)

$$CP = \left\{ 5 \times \left(\frac{1}{0.4 + j0.3} \right) \times 5 \right\} \quad (\text{No } \frac{1}{2} \text{ because of rms})$$



$$= 40 - j30$$

$$\therefore P_{avg} = 40 \text{ W}, \text{ Reactive power} = -30 \text{ Var}$$

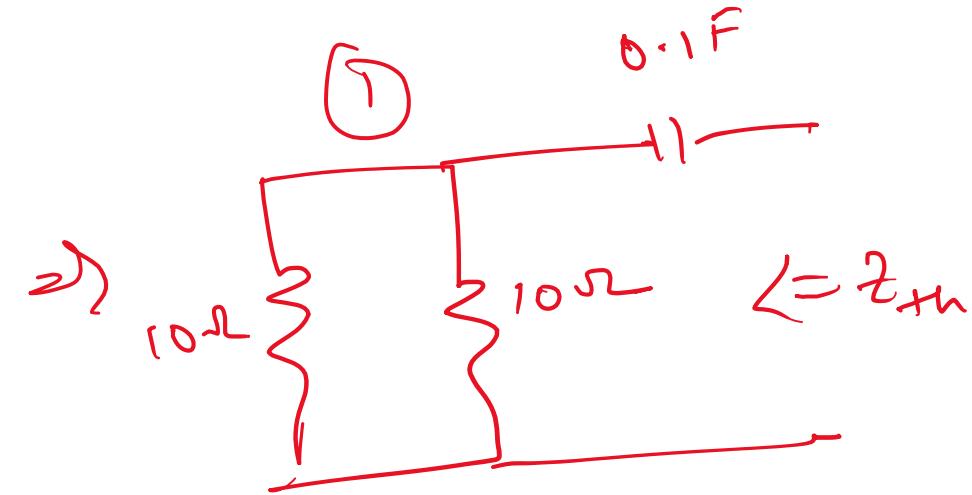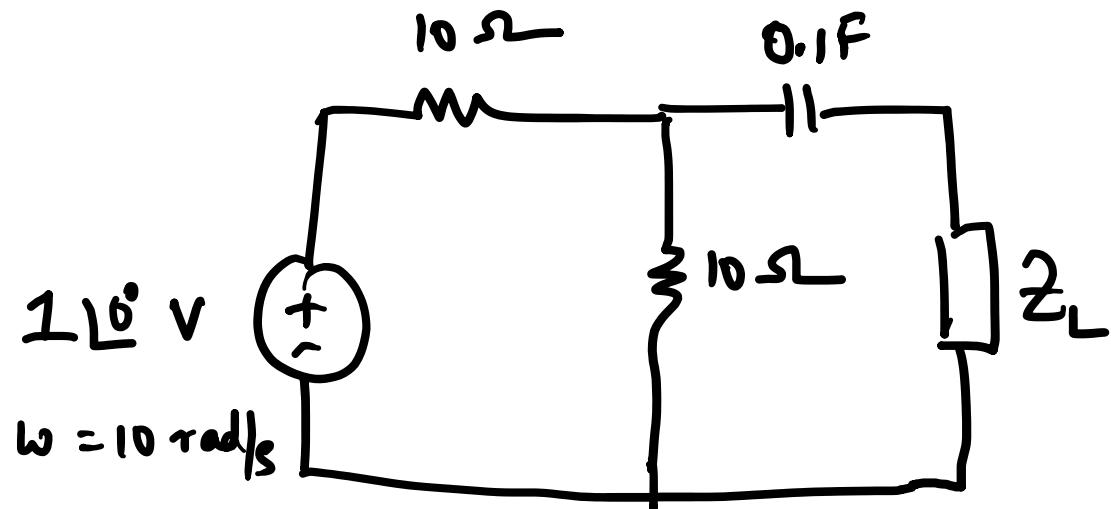(1)

③

$$Z_{th} = [10 \Omega \parallel 10 \Omega] + \frac{1}{j\omega C} = 5 + \frac{1}{j10 \times 0.1} = 5 + \frac{1}{j} = 5 - j$$



∴ $Z_L = Z_{th}^*$ for maximum power transfer

$$\therefore Z_L = (5+j)^2$$

④ $V = 30 e^{+j20^\circ}$, $S = -4 + j5$

$$v(t) = 30 e^{-4t} \cos(5t + 20^\circ) \text{ V} \quad \textcircled{1}$$

⑤ $t = 1 \text{ ms}$

$$v(t) = 30 e^{-4 \times 10^{-3}} \cos\left(5 \times 10^{-3} + 20^\circ \frac{\pi}{180}\right) = 28.027 \text{ V}$$

⑥ $t = 500 \text{ ms}$

$$v(t) = e^{-4 \times 500 \times 10^{-3}} \cos\left(5 \times 500 \times 10^{-3} + 20^\circ \frac{\pi}{180}\right) = -3.88 \text{ V}$$

(5)

$$P_f = 0.5 \text{ lagging}$$

This means current lags behind voltage. So inductive circuit

$$I = \frac{V}{j\omega L}$$

1

$$CP = |CP| \cos \phi - j |CP| \sin \phi$$

$$= \underbrace{|CP| \times 0.5}_{5\omega} - j |CP| \sin \phi$$

$$\Rightarrow |CP| = 5 \times 2 = 10 \text{ } \Omega$$

1

$$\cos \phi = 0.5 \text{ lagging}$$


$$\sin \phi = 0.866$$

$$\text{Reactive power} =$$

$$-10 \times 0.866 = -8.66 \text{ W}$$

Long questions

①

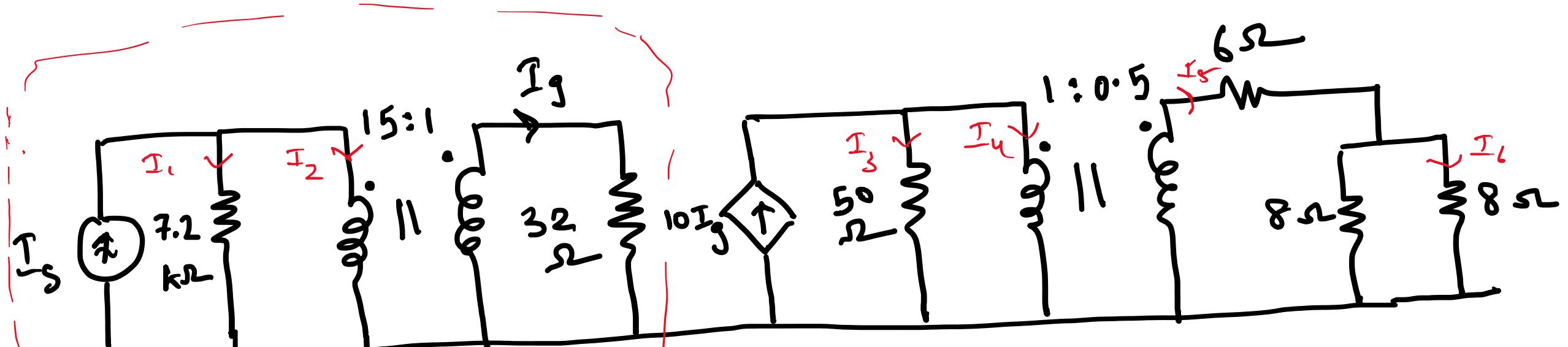

A simplified circuit diagram showing two parallel branches. The top branch contains a $7.2 \text{ k}\Omega$ resistor in series with a I_1 current source. The bottom branch contains a $7.2 \text{ k}\Omega$ resistor in series with a I_2 current source. The total resistance of each branch is $\frac{z_L}{a^2} = \frac{32 \times 15^2}{1} = 7200 \text{ }\Omega$.

$$I_1 = I_S \times \frac{7200}{7200 + 7200} = \frac{I_S}{2} = 16 \text{ A}$$


$$P_1 = \frac{R_S}{2} \times I_1^2 \times z_L = 9.216 \times 10^5 \text{ W}$$

$$I_2 = \frac{I_s \times Z_2}{Z_1 + Z_2} = 32 \times \frac{1}{2} = 16 \text{ A} \quad (1)$$

$$\frac{I_g}{I_2} = \frac{1}{a} \Rightarrow I_g = \frac{1}{a} \times I_2 = 15 \times I_2 = 240 \text{ A} \quad (2)$$

$$P_2 = R \left\{ \frac{1}{2} |I_g|^2 \times Z_2 \right\} = 9.216 \times 10^5 \text{ W} \quad (3)$$

$$10 I_g = 2400 \text{ A}$$

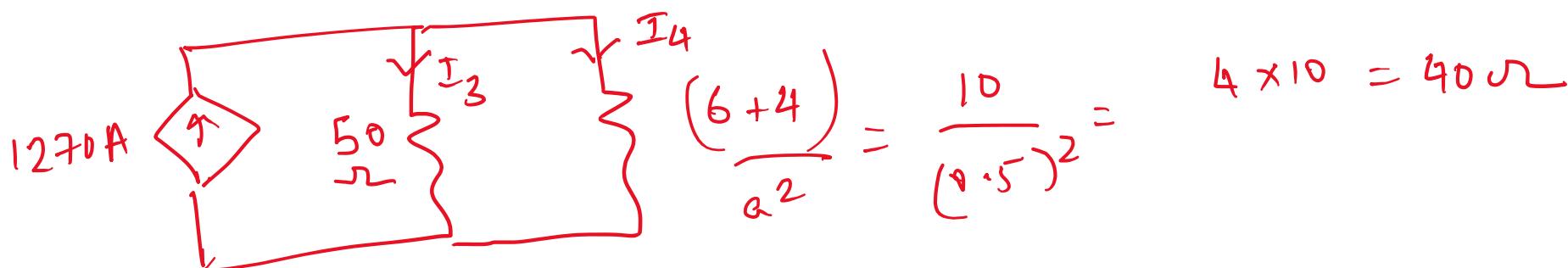


$$I_3 = \frac{10 \times I_g \times 40}{50 + 40} = 1066.67 \text{ A} \quad (1)$$

$$I_4 = \frac{10 \times I_g \times 50}{50 + 40} = 1333.33 \text{ A} \quad (1)$$


$$P_3 = \frac{1}{2} \times [I_3]^2 \times 50 = 28.445 \times 10^5 \text{ W} \quad (1)$$

$$\frac{I_5}{I_u} = \frac{1}{a} \Rightarrow I_5 = \frac{I_u}{0.5}, \quad I_6 = \frac{I_u}{2} = 1333.33 \text{ A} \quad (1)$$

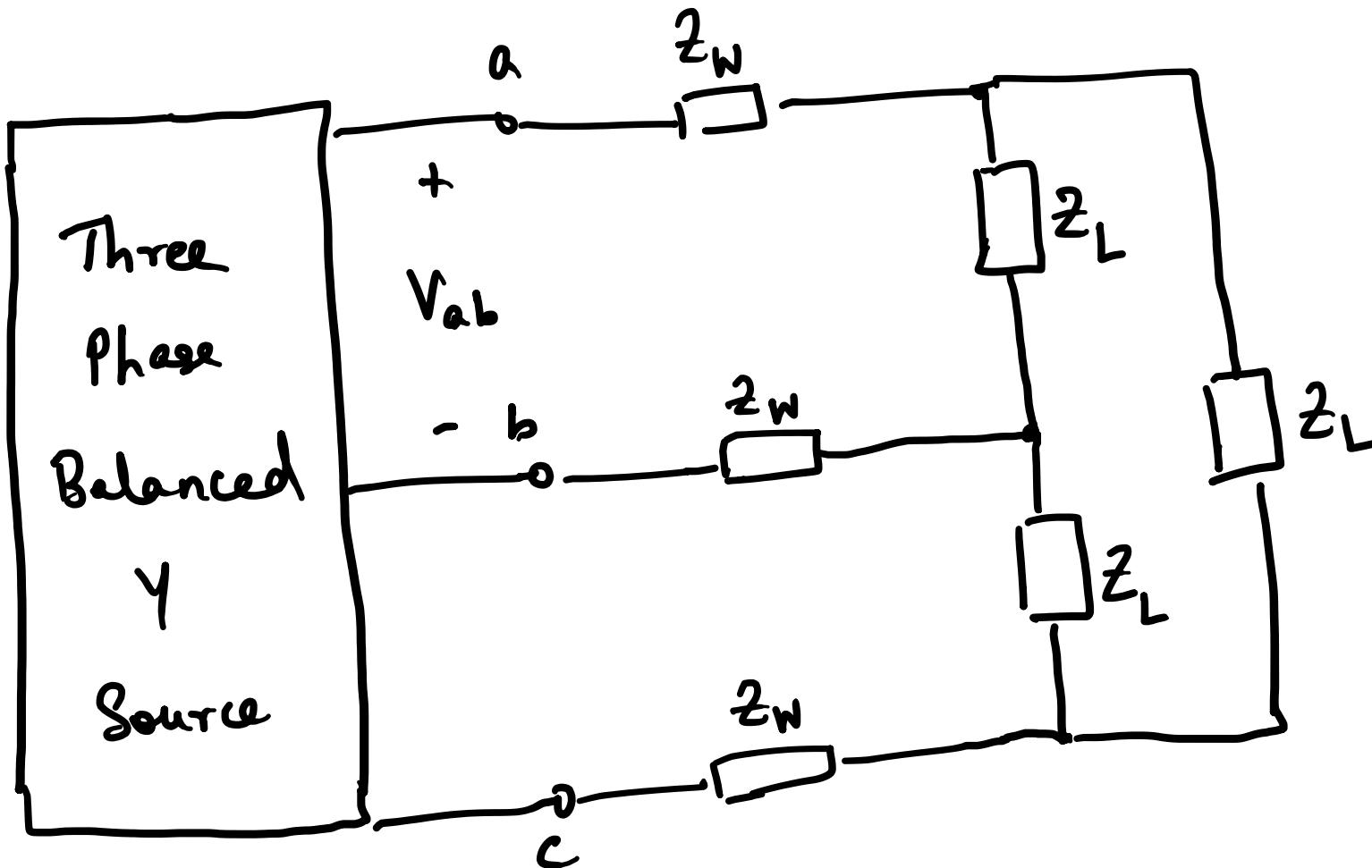
$$P_6 = \frac{1}{2} \times I_6 \times I_6 \times 8 = 7.11 \times 10^6 \text{ W} \quad (1)$$



$$V_{ab} = 380 e^{-j15^\circ} V \Rightarrow V_{an} = \frac{|V_{ab}|}{\sqrt{3}} \angle^{-15^\circ - 30^\circ}$$

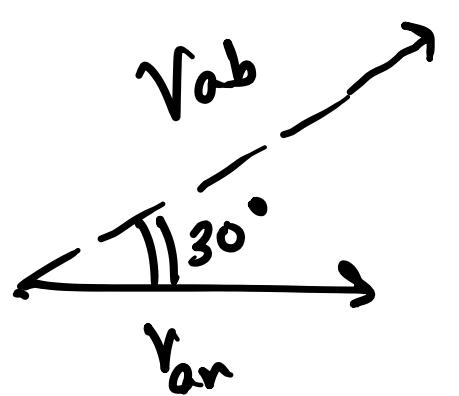

$$= 155 - j 155 \text{ V} \quad (1)$$

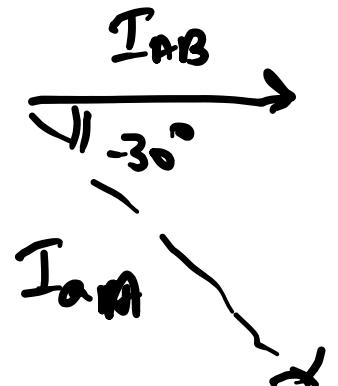


$$\text{Let } I_{OA} = I_0$$

$$I_{AB} = \frac{I_0}{\sqrt{3}} \angle^{50^\circ + 30^\circ} \quad (1)$$

$$= \frac{I_0}{\sqrt{3}} e^{+j30^\circ} A$$

Through Loop
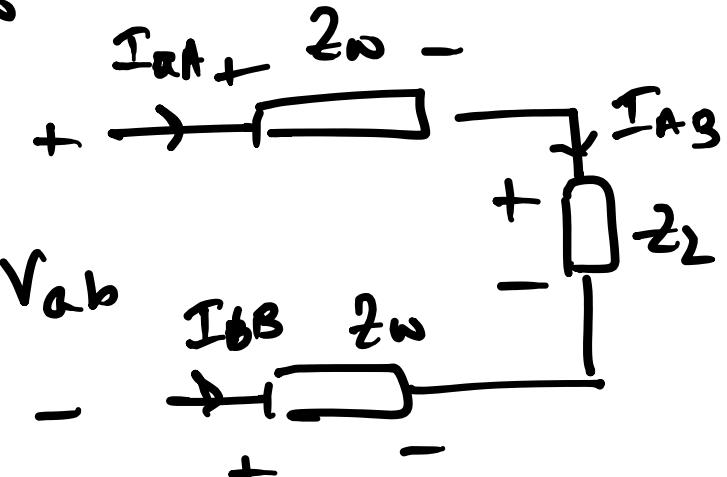
$$+ V_{AB} - I_{AA} Z_w - I_{AB} Z_L + I_{BB} Z_w = 0$$



$$\Rightarrow V_{AB} = I_{AA} Z_w + I_{AB} Z_L - I_{BB} Z_w$$

$$\Rightarrow V_{AB} = I_0 \left[Z_w + \frac{1}{\sqrt{3}} e^{+j30^\circ} Z_L - e^{-j120^\circ} Z_w \right]$$

$$\Rightarrow I_0 = \frac{V_{AB}}{Z_w + \frac{1}{\sqrt{3}} e^{+j30^\circ} Z_L - e^{-j120^\circ} Z_w} = 5.1616 - j 41.866 \text{ A}$$
(1)

$$I_0 = 42.1832 \underbrace{-82.9716}_{\textcircled{1}} \text{ A}$$

$$\rightarrow i_{aA}(t) = 42.1832 \cos(\underbrace{120\pi t}_{\textcircled{1}} - 82.9716^\circ) \text{ A}$$

$$i_{bB}(t) = 42.1832 \cos(120\pi t - 202.9716^\circ) \text{ A}$$

$$i_{cC}(t) = 42.1832 \cos(120\pi t - 322.9716^\circ) \text{ A}$$

(a)

$$I_{AB} = \frac{\overline{I_{aA}} + j30^\circ}{\sqrt{3}} = \frac{42.1832 \underbrace{-52.9716}_{\textcircled{1}}}{\sqrt{3}} = 24.3552 \underbrace{-52.9716}_{\textcircled{1}} \text{ A}$$

$$I_{BC} = 24.3552 \underbrace{-172.9716}_{\textcircled{1}} \text{ A}$$

$$I_{CA} = 24.3552 \underbrace{-292.9716}_{\textcircled{1}} \text{ A}$$

✓ load currents (b)

$$P_{ms}(t) = V_{an}(t) i_{an}(t) + V_{bn}(t) i_{bB}(t) + V_{cn}(t) i_{cB}(t)$$

(7)

$$= 9.2453 \times 10^3 \cos(120\pi t - 45^\circ) \cos(120\pi t - 82.9716^\circ) +$$

$$9.2453 \times 10^3 \cos(120\pi t - 45^\circ - 120^\circ) \cos(120\pi t - 82.9716 - 120^\circ) +$$

$$9.2453 \times 10^3 \cos(120\pi t - 45^\circ - 240^\circ) \cos(120\pi t - 82.9716 - 240^\circ) \text{ kW}$$

$$= \frac{9.2453 \times 10^3}{2} \left[\cos(240\pi t - 127.9716^\circ) + \cos(37.9716^\circ) \right]$$

$$= 13.868 \cos(240\pi t - 127.9716^\circ) + 10.9323 \text{ kW}$$

$$(d) P_L = \frac{3}{2} \times \text{Re} \left\{ I_{AB} \times Z_L \times I_{AB}^* \right\} = 10.677 \text{ kW} \quad (1)$$

$$(e) P_W = \frac{3}{2} \times \text{Re} \left\{ I_0 \times Z_W \times Z_W^* \right\} = 266.9131 \text{ W} \quad (1)$$

$$Z_C = -j^{0.4} \Omega$$

$$Z_L = +j^{10} \Omega$$

$$Z_{L_2} = +j^{10} \Omega$$


$$M = k\sqrt{L_1 L_2} = 0.5 \times 2 \\ = 1$$

$$Z_M = +j^5 \Omega$$

$$Z_{\text{Load}} = j^{50} \Omega$$

M=Same

(2)

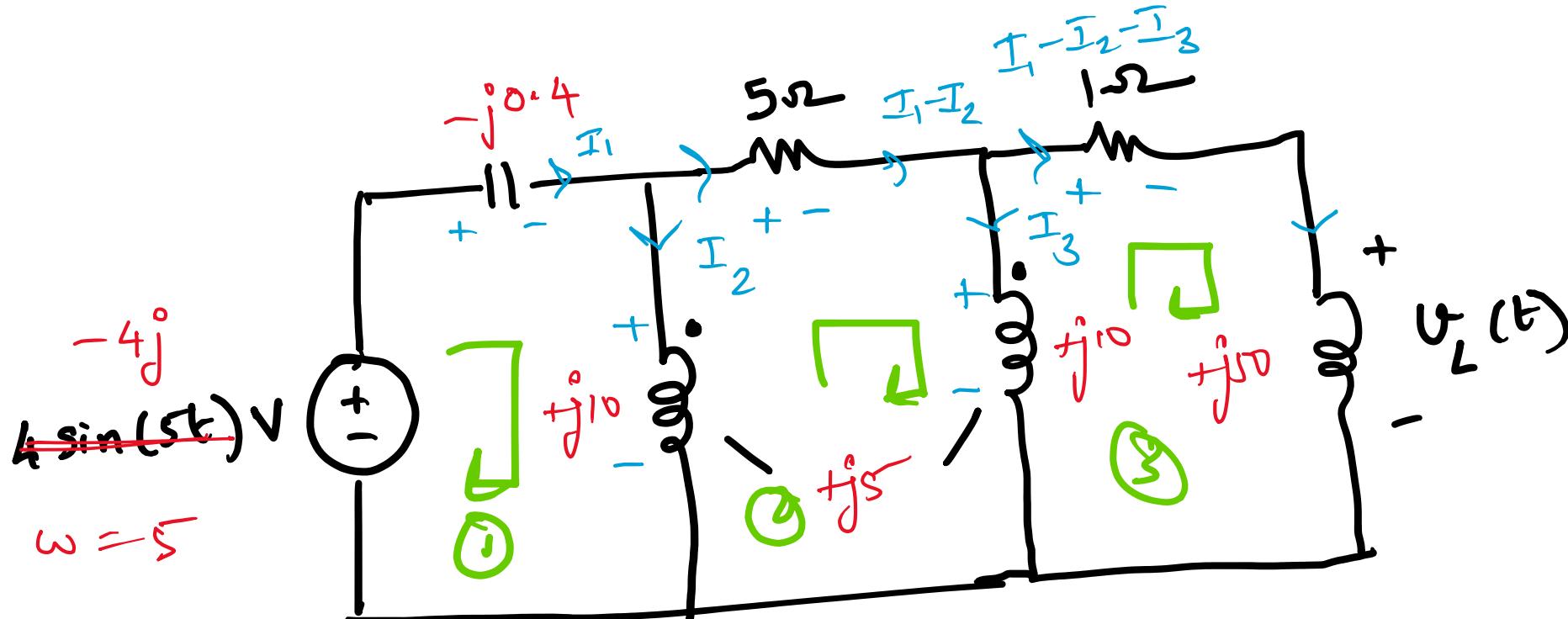

Loop 1

$$+V_S - I_1(-j^{0.4}) - I_2(+j^{10}) - I_3(+j^5) = 0 \quad \textcircled{2}$$

$$\Rightarrow I_1(-j^{0.4}) + I_2(+j^{10}) + I_3(+j^5) = V_S = -4j \quad \textcircled{1}$$

Loop -2

$$+I_2(+j^{10}) + I_3(+j^5) - (I_1 - I_2)(s^-) - I_3(+j^{10}) - I_2(+j^5) = 0$$

$$\Rightarrow I_1(-s) + I_2(+j^{10} + s^- - j^5) + I_3(+j^5 - j^{10}) = 0 \quad \textcircled{2}$$

$$\Rightarrow I_1(-s) + I_2(s + j^5) + I_3(-j^5) = 0 \quad \textcircled{2}$$

Loop-3

$$+ I_3(j^{10}) + I_2(+j^5) - (I_1 - I_2 - I_3)(1) - j^{50}(I_1 - I_2 - \frac{I}{3}) = 0$$

$$I_1(-1 - j^{50}) + I_2(+j^5 + 1 + j^{50}) + I_3(+j^{10} + 1 + j^{50}) = 0 \quad (2)$$

$$\Rightarrow I_1(-1 - j^{50}) + I_2(+j^{55} + 1) + \frac{I}{3}(+j^{60} + 1) = 0 \quad (3)$$

$$I_1 = -0.5699 - j^{10} \cdot 11.67 \text{ A}$$

$$I_2 = -0.3418 + j^{10} \cdot 0.732 \text{ A}$$

$$I_3 = -0.1620 - j^{10} \cdot 15.49 \text{ A}$$

$$I_L = I_1 - I_2 - I_3 = -0.0661 - j^{10} \cdot 0.2501 \text{ A}$$

$$V_L = I_L \times Z_{\text{load}} = 1.2489 - j3.3037 \text{ V}$$

$$|V_L| = 3.5319 \text{ V}$$

$$\angle V_L = -69.2914^\circ$$

(2)

$$\Rightarrow \theta_L(t) = 3.35319 \cos(5t - 69.2914^\circ) \text{ V}$$