

BE END SEM EXAM RUBRIC

PART (I) :-

SOL(1) :-

Voltage Magnification: In Series Resonance of R, L & C circuit, the voltage across inductor 'OR' voltage across capacitor is greater than the source voltage. This phenomenon is called as Voltage Magnification.


→ (1 Point)

Current Magnification: In Parallel Resonance of R, L & C circuit, the current in an inductor OR the current in capacitor is greater than the source current. This phenomenon is called as Current Magnification.

→ (1 Point)

SOL(2) :-

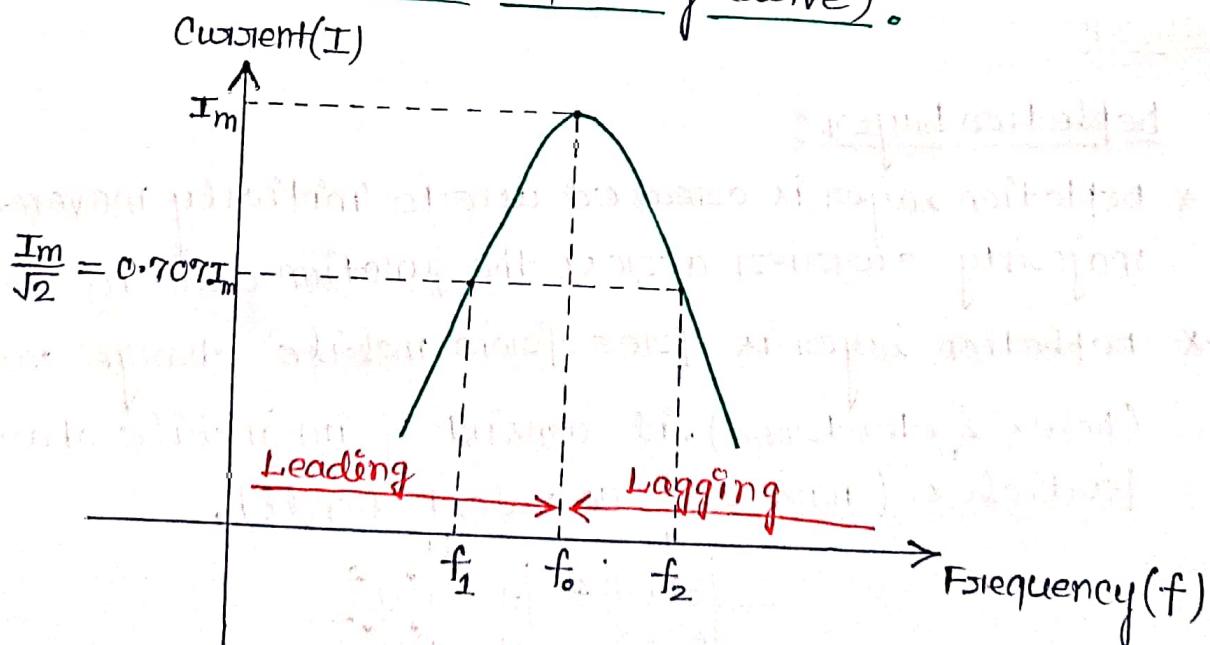Resonance Curve (Current vs Frequency Curve):




where, f_0 = Resonance frequency

f_1 & f_2 = Half Power frequency, 'OR' 3-dB Points

f_1 = Lower cut off frequency
 f_2 = Upper cut off frequency
 I_m = Maximum current

→ (1 Point)

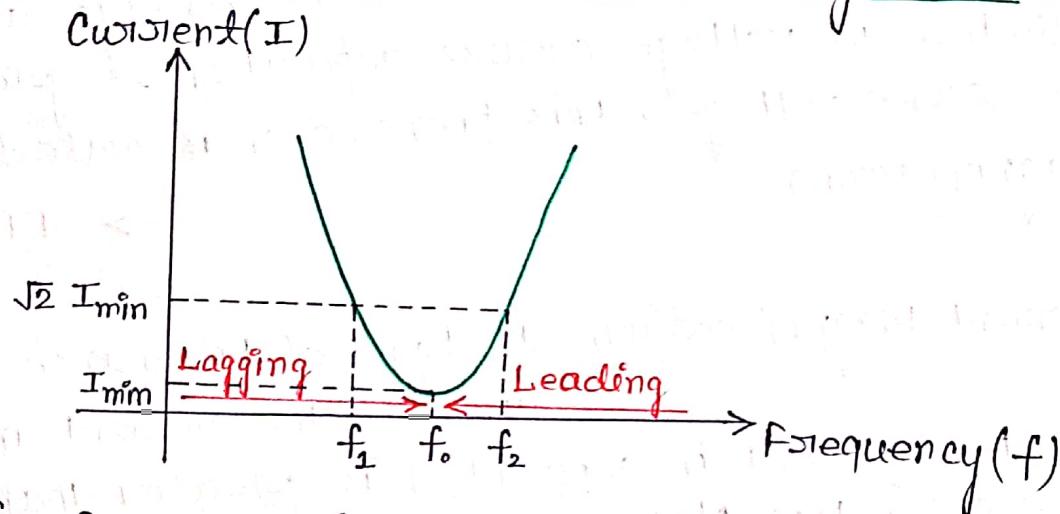Anti Resonance Curve (Current vs frequency curve):



where, f_0 = Resonance frequency

f_1 = Lower cut off frequency

f_2 = Upper cut off frequency


I_{min} = Minimum current

→ (1 Point)

SOL(3):

Depletion Layer:

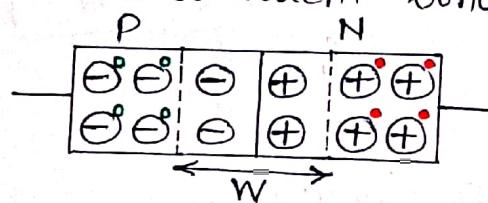- * Depletion layer is created due to initial movement of majority carriers across the junction due to diffusion.
- * Depletion layer is free from mobile charge carriers (holes & electrons), it consists of immobile charge particles (ions and co-valent bonds).



W = Depletion layer width

→ (1 Point)

Effect of Biasing on Depletion Width:

* Case(I): Forward Biasing

When P-N Junction is forward bias, then the width of depletion layer slightly decreases. → (0.5 Point)

* Case(II): Reverse Biasing

When P-N Junction is reverse bias then the width of depletion layer slightly increases. → (0.5 Point)

SOL(4):

Dark Current: When a reverse bias Photo Diode is kept under darkness then the Photo Diode will be working as normal diode & the current flowing through this is called as dark current.

→ (1 Point)

* Photo diode is work under Reverse Bias (RB) condition. → (0.5 Point)

* Solar cell is work under Unbiased Mode. → (0.5 Point)

SOL(5):

D₁ : ON


D₂ : OFF

D₃ : OFF

→ (2 Point)

SOL(6):

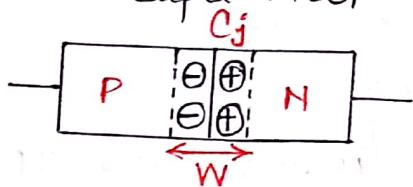- * Yes, Diode can be used as variable capacitor.
- * In a P-N junction, the depletion layer will be working as a parallel plate capacitor.



Here, Junction Capacitance, $C_j = \frac{A\epsilon}{W}$ Farad

where A = Junction area

W = Depletion layer width

$$C_j \propto A$$

$$C_j \propto (1/W)$$

- * Hence by varying Junction area 'OR' width of depletion layer, we can vary Junction capacitance.

→ (2 Point)

SOL(7):

Direct Band Gap (DBG) Semiconductor

- * During recombination, most of the energy is released in form of light.

- * During recombination, most of free e⁻'s falling from CB will directly fall into VB & hence the name is DBG-SC.

- * GaAs, GaSb, GaN, InAs, InSb, ZnS, ZnSe, CdS, CdSe, InP

Indirect Band Gap (IBG) Semiconductor

- * During recombination, most of the energy is released in the form of heat.

- * During recombination, most of the free e⁻'s falling from CB will go into intermediate level & then fall into VB & hence the name is IBG-SC.

- * Si, Ge, AlP, AlSb, PbS, PbSe, GaP

→ (2 Point)


DBG Semiconductor

- * The energy of the falling \bar{e} 's changes (both KE & PE changes)
- * No change in direction of the falling \bar{e} 's ($cB \rightarrow VB$)
- * No change in the path of falling \bar{e} 's.
- * The \bar{e} 's can release energy with or without a change in momentum of the falling \bar{e} 's.
- * Relatively smaller carrier lifetime.

IBGI Semiconductor

- * The energy of the falling \bar{e} 's changes (both KE & PE changes)
- * No change in the direction of the falling \bar{e} 's ($cB \rightarrow VB$)
- * The path of falling \bar{e} 's changes.
- * No \bar{e} 's can release the energy without a change in momentum of the falling \bar{e} 's.
- * Relatively longer carrier lifetime.

SOL(B):

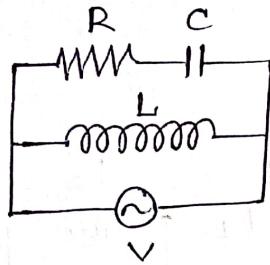

$$\begin{aligned}
 \text{Equivalent impedance } (Z_{eq}) &= (R - jX_C) \parallel (jX_L) \\
 &= \frac{(R - jX_C)(jX_L)}{(R - jX_C + jX_L)} = \frac{(jRX_L + X_C X_L)}{R + j(X_L - X_C)} \\
 &= \frac{[jRX_L + X_C X_L][R - j(X_L - X_C)]}{[R + j(X_L - X_C)][R - j(X_L - X_C)]}
 \end{aligned}$$

For resonance freq (f_0), $\text{Img}(Z_{eq}) = 0$

$$\frac{R^2 X_L - X_C X_L (X_L - X_C)}{R^2 + (X_L - X_C)^2} = 0$$

$$R^2 X_L = X_C X_L (X_L - X_C)$$


$$R^2 = \frac{1}{\omega C} \left(\omega L - \frac{1}{\omega C} \right)$$

$$\therefore f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{(LC - R^2 C^2)}} \text{ Hz.}$$

→ (2 Point)

Part (II)

SOL(1)

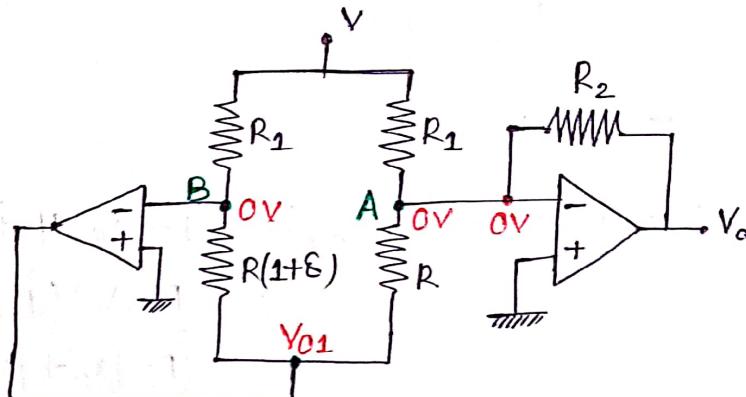

KCL at node 'B' —

$$\frac{0-V}{R_1} + \frac{0-V_{01}}{R(1+\delta)} = 0$$

$$\therefore V_{01} = -\frac{R(1+\delta)}{R_1} V \quad \rightarrow (\exists \text{ Point})$$


KCL at node 'A' —

$$\frac{0-V}{R_1} + \frac{0-V_0}{R_2} + \frac{0-V_{01}}{R} = 0$$



$$\therefore V_0 = \left(\frac{R_2}{R_1} \delta V \right) \quad \rightarrow (\exists \text{ Point})$$

SOL(2)

Equivalent circuit at $t = (-2)$ sec

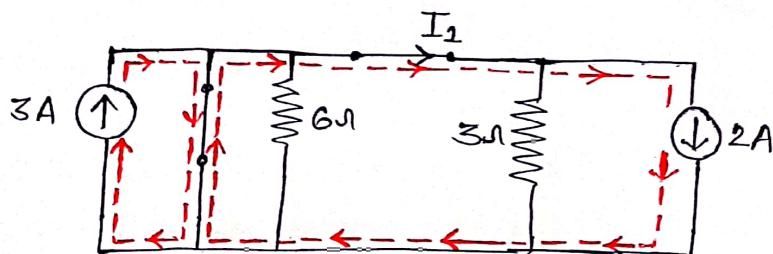


$$\therefore I_1 = 2A$$

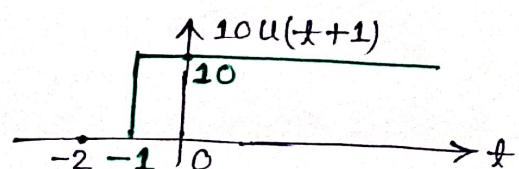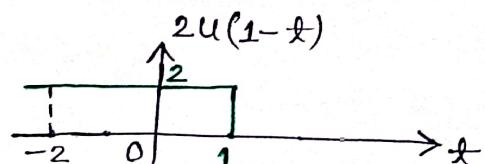

$\rightarrow (6 \text{ Point})$

SOL(3) :

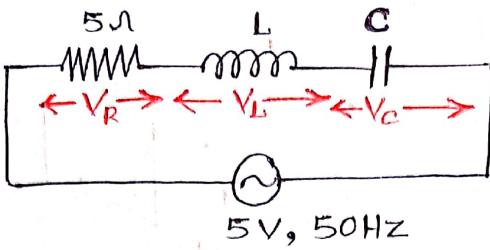

Given - $V_L = V_C = 2V_R$ (showing Resonance condition)

We know that at resonance, $X_R = X$

$$\therefore V_R = 5 \text{ Volt}$$

$$\therefore V_L = V_C = 10 \text{ Volt}$$

For Series Resonance, Quality factor (Q) = $\frac{X_L 'OR' X_C}{R} = \frac{V_L 'OR' X_C}{V}$

$$\therefore Q = \frac{V_L 'OR' X_C}{V} = \frac{10}{5} = 2$$


$$Q = \frac{X_L}{R} = \frac{\omega L}{R}$$

$$2 = \frac{50 \times L \times 2\pi}{5}$$

$$\therefore L = (1/10\pi) \text{ H} \rightarrow (\text{G Point})$$

SOL(4) :

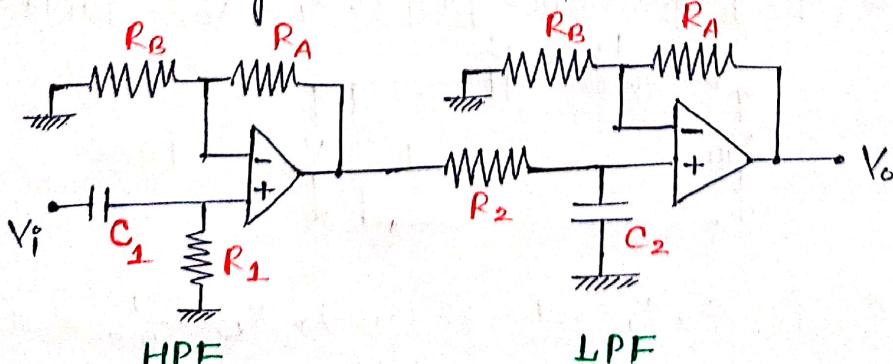Case(I) : BPF using op-amp, capacitors & resistors




$$f_L = \left(\frac{1}{2\pi R_1 C_1} \right) \text{ Hz}$$

$$f_H = \left(\frac{1}{2\pi R_2 C_2} \right) \text{ Hz}$$


where, $f_H > f_L$

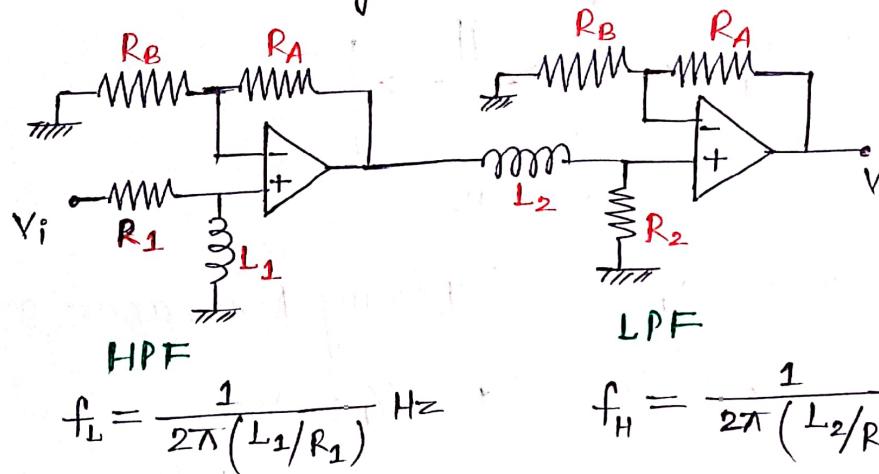Case(II): BPF using Op-amp, Inductor & Resistor




where $f_H > f_L$

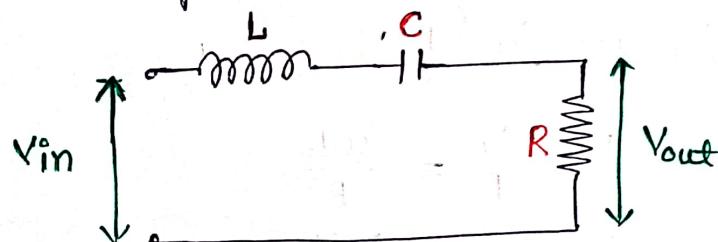
* It is possible to make BPF using only $R, L \& C$ (Passive filters). One of the example is - RLC series BPF



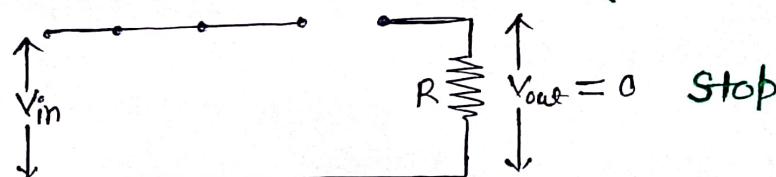
Case(I): at $f=0 \text{ Hz}$, $X_L=\omega L=0$ (S.C.), $X_C=\frac{1}{\omega C}=\infty$ (O.C.)



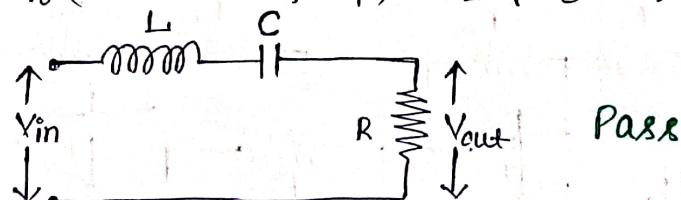Case(II): at $f=f_0$ (resonance freq.), $X_L \& X_C = \text{finite value}$



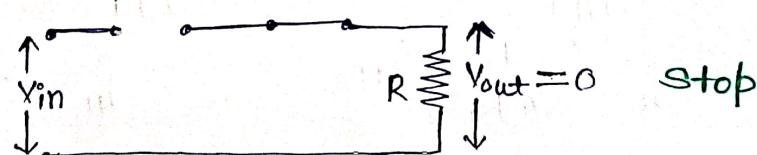
Case(III): at $f=\infty$, $X_L=\omega L=\infty$ (O.C.), $X_C=\frac{1}{\omega C}=0$ (S.C.)



So, this is Band Pass filter (BPF).


SOL(5):

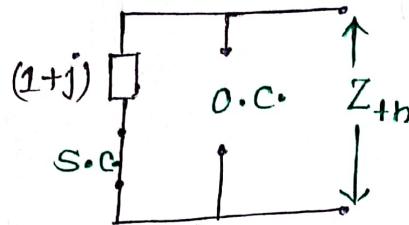Case(I): To find Thevenin Resistance (Z_{th})




$$\therefore Z_{th} = (1+j) = \sqrt{2} / 45^\circ \Omega \rightarrow \text{(2 Point)}$$

Case(II): To find Norton Current (I_N)

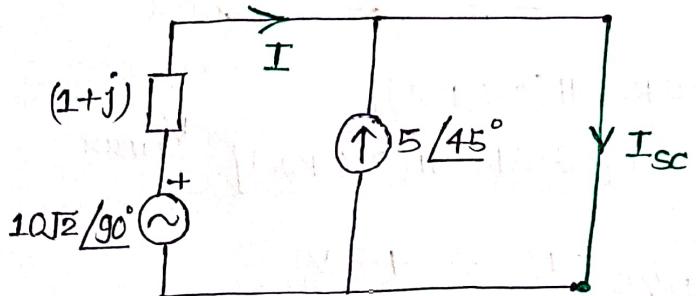

$$\begin{aligned} \therefore I_{sc} &= I + 5 / 45^\circ = \frac{10\sqrt{2} / 90^\circ}{\sqrt{2} / 45^\circ} + 5 / 45^\circ \\ &= 10 / 45^\circ + 5 / 45^\circ = 15 / 45^\circ A \rightarrow \text{(2 Point)} \end{aligned}$$

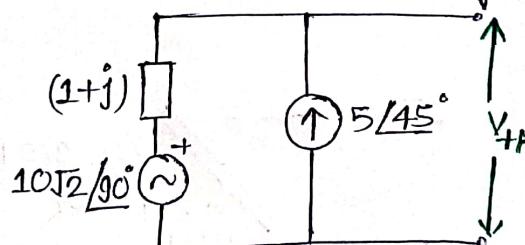Case(III): To find Thevenin Voltage (V_{th})



$$\frac{V_{th} - 10\sqrt{2} / 90^\circ}{\sqrt{2} / 45^\circ} = 5 / 45^\circ$$


$$\therefore V_{th} = 15\sqrt{2} / 90^\circ \text{ Volt} \rightarrow \text{(2 Point)}$$

SOL(6):

Case(I): First Positive half cycle of input voltage

D₁ → OFF

D₂ → ON

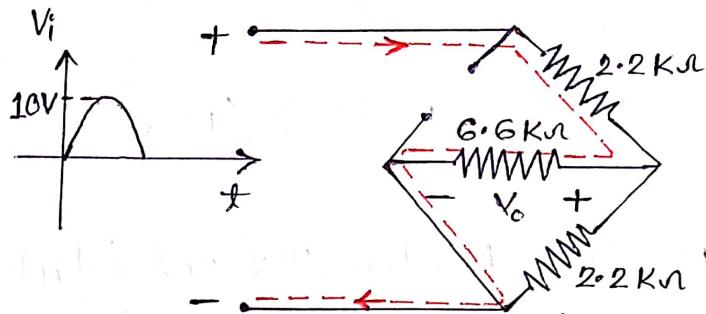

$$\therefore V_{o\max} = \frac{[(6.6 \text{ k}\Omega) \parallel (2.2 \text{ k}\Omega)]}{2.2 \text{ k}\Omega + [(6.6 \text{ k}\Omega) \parallel (2.2 \text{ k}\Omega)]} V_{i\max}$$


$$= \frac{0.75}{1+0.75} \times 10 = 4.3 \text{ V}$$



Case(II): First Negative half cycle of input voltage


D₁ → ON

D₂ → OFF

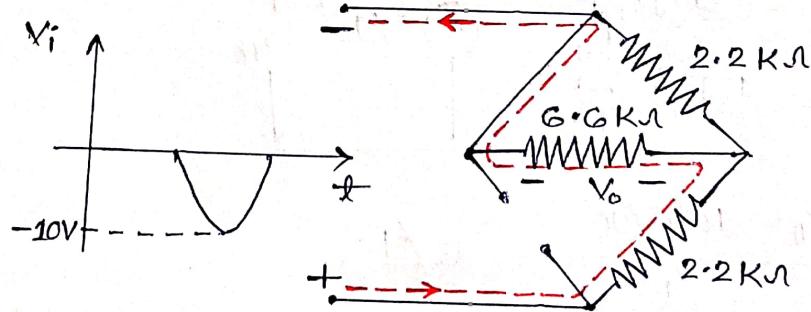


$$\therefore V_{o\max} = \frac{[(6.6 \text{ k}\Omega) \parallel (2.2 \text{ k}\Omega)]}{2.2 \text{ k}\Omega + [(6.6 \text{ k}\Omega) \parallel (2.2 \text{ k}\Omega)]} V_{i\max}$$
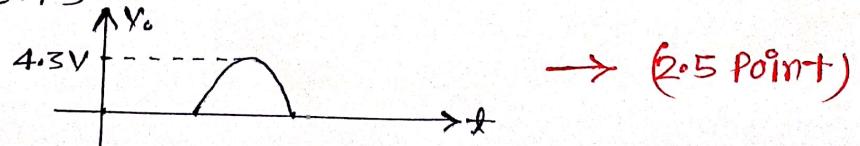
$$= \frac{0.75}{1+0.75} \times 10 \text{ V} = 4.3 \text{ V}$$




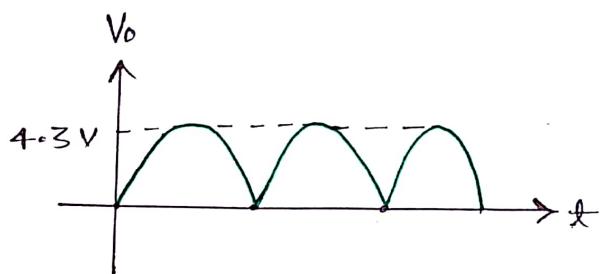still the polarity of output voltage is in the same direction. So, net output of the circuit will be a full rectified wave.



→ (1 Point)

SOL(7)

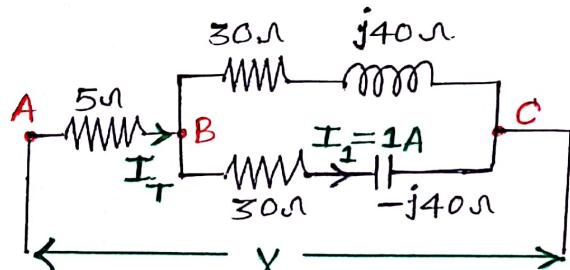

$$I_1 = I_T \times \left(\frac{30 + j40}{30 + j40 + 30 - j40} \right)$$

$$I_1 = I_T \times \frac{50 \angle \tan^{-1}(4/3)}{60}$$

$$I_T = \frac{60}{50 \angle \tan^{-1}(4/3)} = 1.2 \angle \tan^{-1}(-4/3) \text{ A}$$

$$\therefore V_{AB} = 5 \times I_T = 6 \angle \tan^{-1}(-4/3) \text{ V}$$

$$\therefore V_{BC} = 1 \times (30 - j40) = 50 \angle \tan^{-1}(-4/3) \text{ V}$$

$$\therefore V = V_{AB} + V_{BC}$$

$$= 6 \angle \tan^{-1}(-4/3) + 50 \angle \tan^{-1}(-4/3)$$

$$= 56 \angle \tan^{-1}(-4/3) \text{ Volt}$$

→ (6 Point)