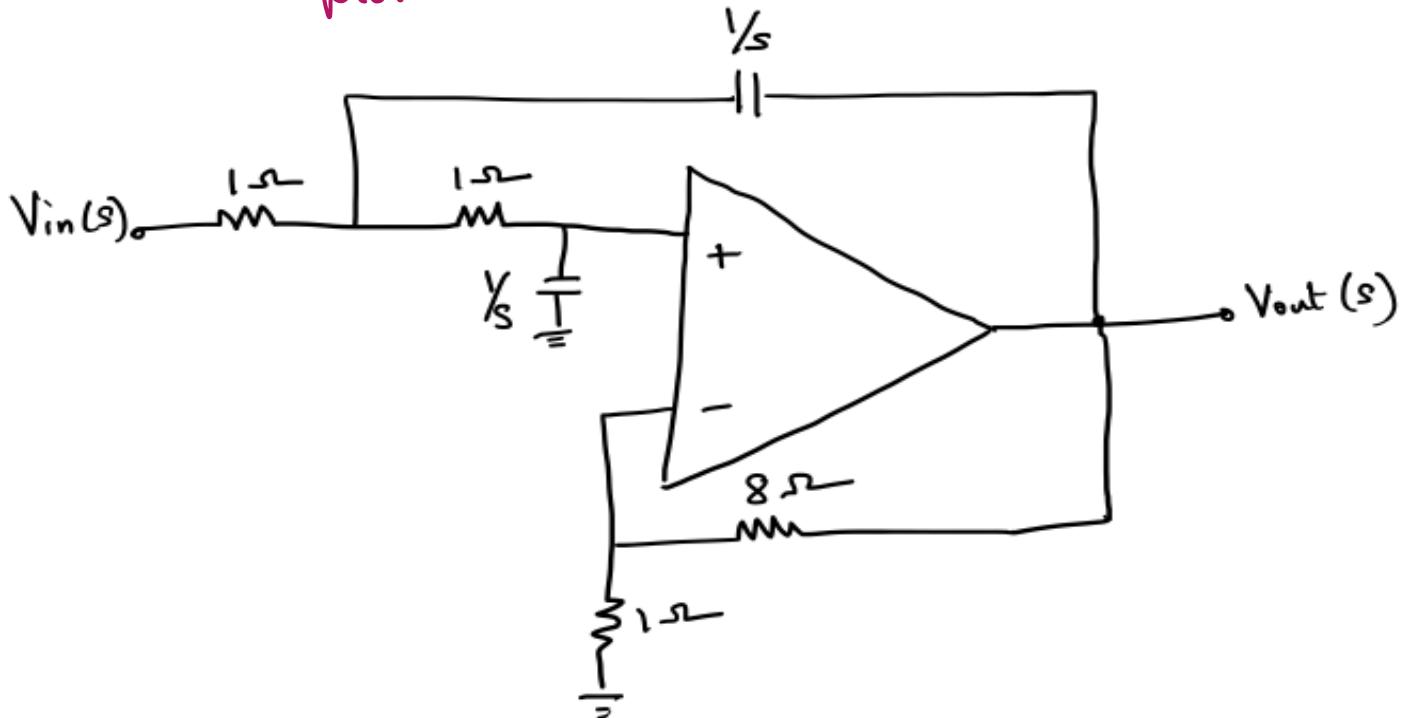


Quiz 4 (20 marks)

Consider the circuit shown below with an ideal op-amp.


1. (3 marks) Describe the type of filter (order, whether its active or passive, lpf/hpf/bpf-bsf) 1 + 1 + 1 marks
2. (10 marks) Plot the magnitude response of the circuit $H(s) = \left\| \frac{V_{out}(s)}{V_{in}(s)} \right\|$ on the semi-log sheet attached to the answer sheet. 5 marks
mag. eq'n → 2 marks
plot → 3 marks
3. (7 marks) Draw the phase response of the above circuit on the semi-log sheet. phase eq'n → 2 marks
plot → 5 marks



Quiz 4 (20 marks)

Consider the circuit shown below with an ideal op-amp.


- (3 marks) Describe the type of filter (order, whether its active or passive, lpf/hpf/bpf-bsf) **1 + 1 + 1**
- (10 marks) Plot the magnitude response of the circuit $H(s) = \left\| \frac{V_{out}(s)}{V_{in}(s)} \right\|$ on the semi-log sheet attached to the answer sheet. **5 marks** **mag eq $\rightarrow 2m$**
- (7 marks) Draw the phase response of the above circuit on the semi-log sheet. **plot $\rightarrow 3m$.**
p'nose eq $\rightarrow 2m$
plot $\rightarrow 5m$

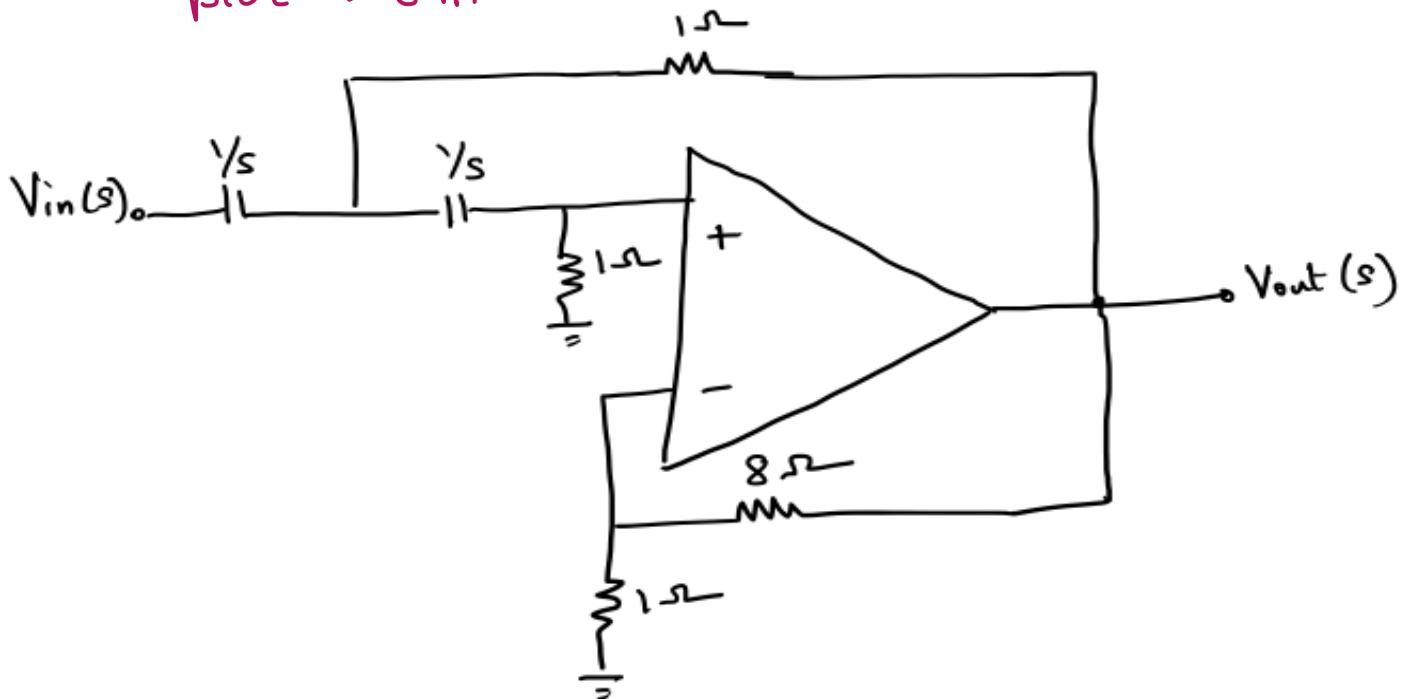

Quiz 4 (20 marks)


Consider the circuit shown below with an ideal op-amp.

1. (3 marks) Describe the type of filter (order, whether its active or passive, lpf/hpf/bpf-bsf) **1+1+1**
2. (10 marks) Plot the magnitude response of the circuit $H(s) = \left| \frac{V_{out}(s)}{V_{in}(s)} \right|$ on the semi-log sheet attached to the answer sheet. **mag eq $\rightarrow 2m$**
plot $\rightarrow 3m$
3. (7 marks) Draw the phase response of the above circuit on the semi-log sheet.
phase eqn $\rightarrow 2m$.
plot $\rightarrow 5m$.

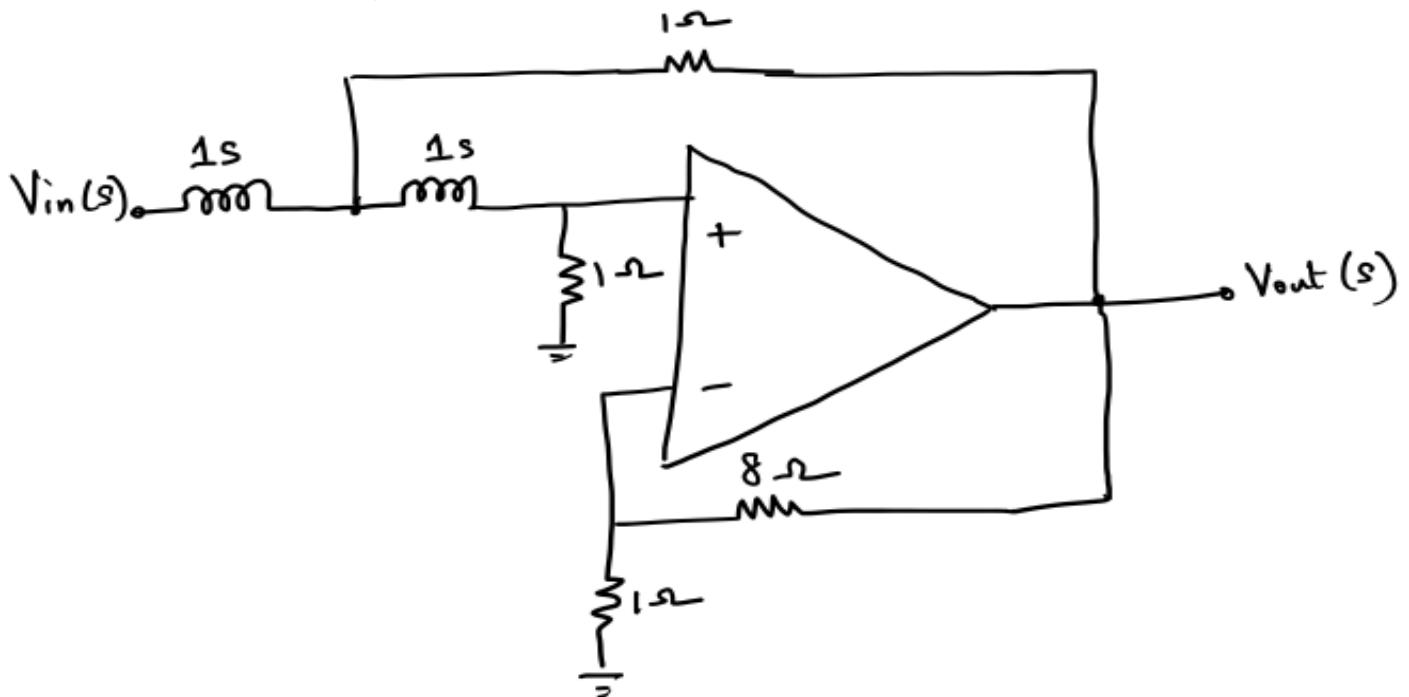

Quiz 4 solution set 1

Set 1

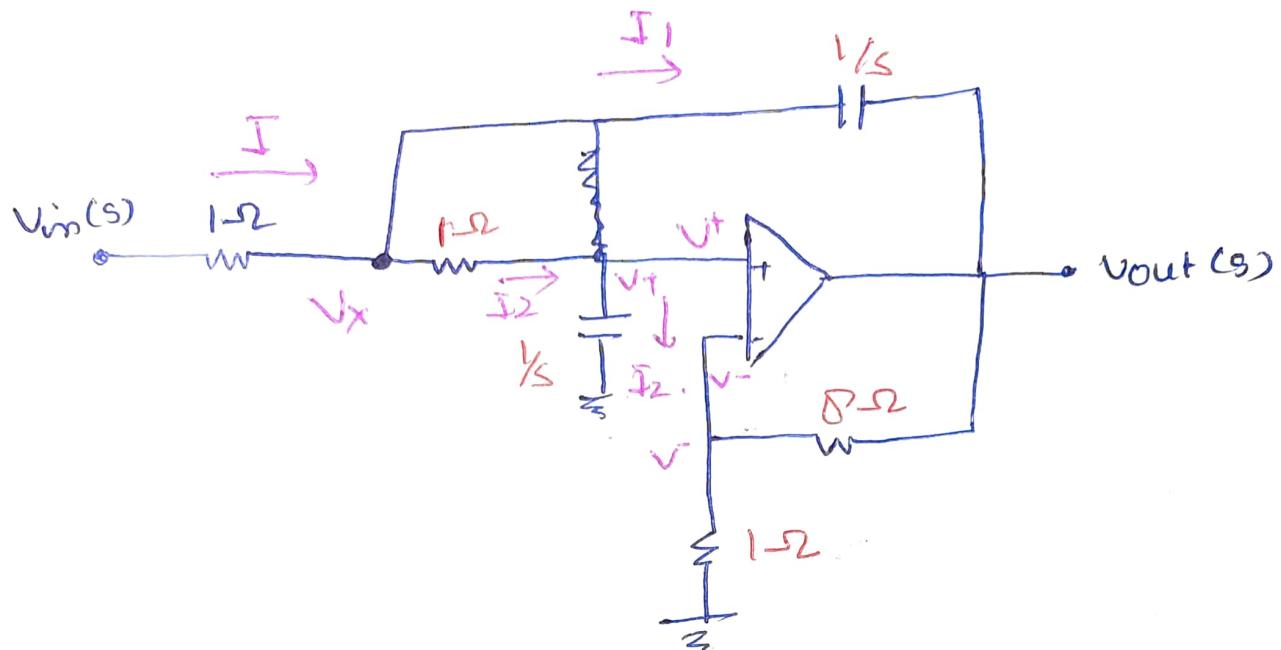

\therefore it is an ideal op-amp

\therefore we can write,

$$\boxed{V^- = V^+ = V_{out} \left(\frac{1}{g} \right) \stackrel{\approx}{=} \frac{V_{out}}{g}} \rightarrow ①.$$

↳ voltage divider rule.

$$\text{Now, } I_2 = \frac{V_n - V^+}{R_2} = \frac{V^+ - 0}{Y_s} = sV^+$$

$$\Rightarrow V_n = sV^+ + V^+$$

$$\Rightarrow \boxed{V_n = (1+s)V^+} \rightarrow ②$$

Now applying KCL,

$$\frac{V_m - V_n}{L} = \frac{V_n - V_{out}}{Y_s} + \frac{V_n}{1/s + 1}$$

$$\Rightarrow V_m - V_n = sV_n - sV_{out} + \frac{sV_n}{1+s}$$

$$\Rightarrow V_m - V_n = \left[s + \frac{s}{1+s} \right] V_n - sV_{out}$$

$$\Rightarrow V_m^o - V_n = \left(\frac{s^2 + s + s}{s+1} \right) V_n - sV_{out}$$

$$\Rightarrow V_m^o = \left[\frac{s^2 + 3s + 1}{s+1} \right] V_n - sV_{out}$$

from ②

$$V_m^o = \frac{s^2 + 3s + 1}{s+1} \times (s+1) \times V^+ - sV_{out}$$

$$\Rightarrow V_m^o = \left(\frac{s^2 + 3s + 1}{s+1} \right) V_{out} - sV_{out}$$

$$\Rightarrow V_m^o = V_{out} \left[\frac{s^2 + 3s + 1 - 9s}{s} \right]$$

$$\Rightarrow \boxed{\frac{V_{out}}{V_m^o} = \frac{9}{s^2 - 6s + 1}} \rightarrow \boxed{H(s) = \frac{9}{s^2 - 6s + 1}}$$

Now, we can write,

$$H(s) = \frac{9}{(s - 5.82)(s - 0.17)}$$

$$\Rightarrow H(j\omega) = \frac{9}{(j\omega - 5.82)(j\omega - 0.17)}$$

\therefore Poles $\rightarrow \omega_1 = 5.82 \text{ rad/s}$
 $\omega_2 = 0.17 \text{ rad/s.}$

Now $|H(\omega)| = \frac{9}{\sqrt{(1-\omega^2)^2 + 36\omega^2}}$ $\xrightarrow{\text{indB}} 20 \log_{10} \left(\frac{9}{\sqrt{K}} \right) + \text{dB}$

$$\angle H(\omega) = -\tan^{-1} \left[\frac{6\omega}{1-\omega^2} \right]$$

ω	$ H(\omega) \text{ dB}$	$\angle H(\omega)$
0.01	19.08	3.43°
0.1	17.87	31.22°
0.17	16.16	46.4°
5.82	-14.53	-46.73°
10	-26.35 -16.35	-31.22°
100	-36.35	-30.43°


(a) we can observe and say that it is —

- ① Active filter
- ② Second order
- ③ low pass filter.

Magnitude plot.
 $|H(\omega)|$

EWeb


TITLE	
NAME	DATE

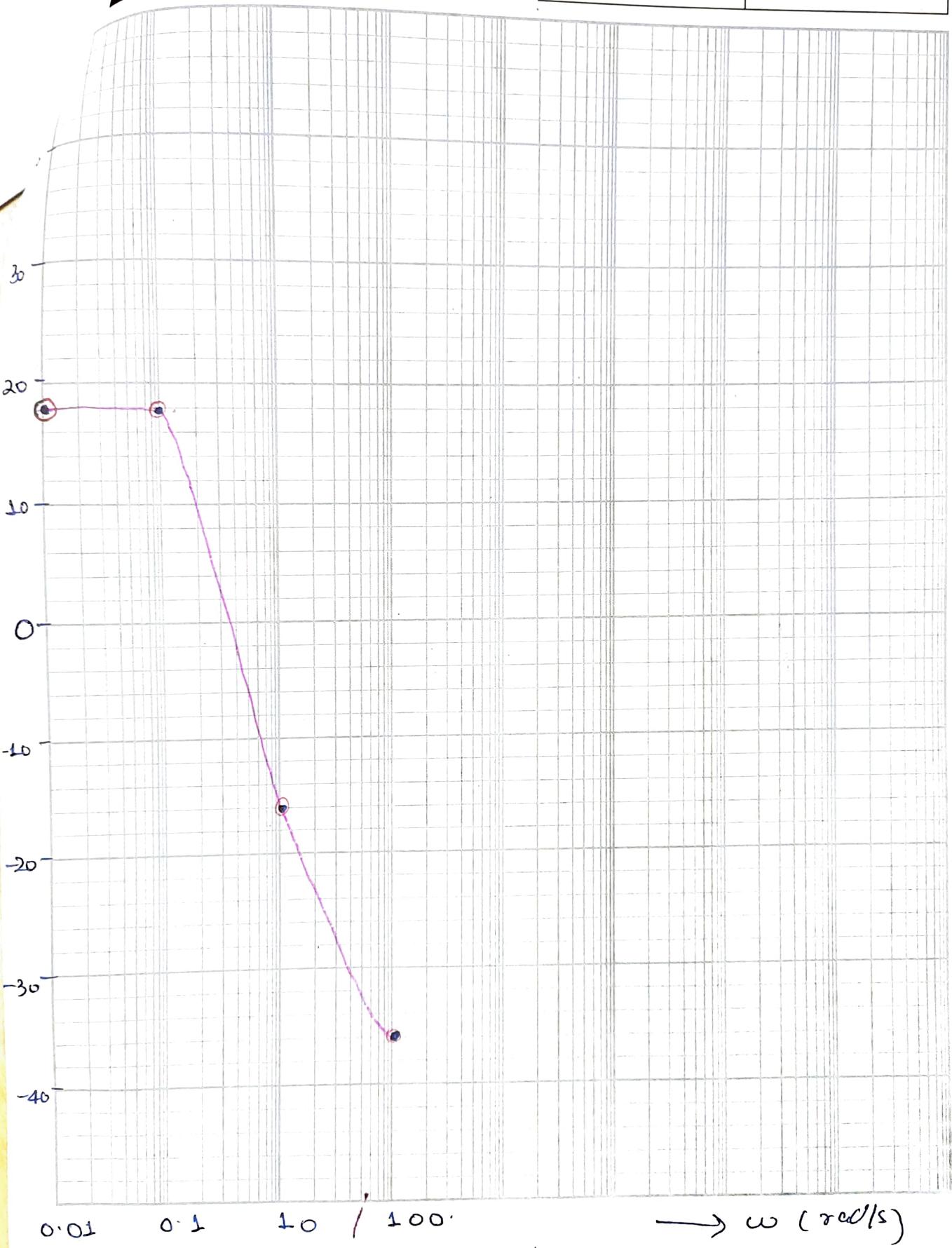

$\angle H(\omega)$


Web Phase Plot

TITLE	
NAME	DATE

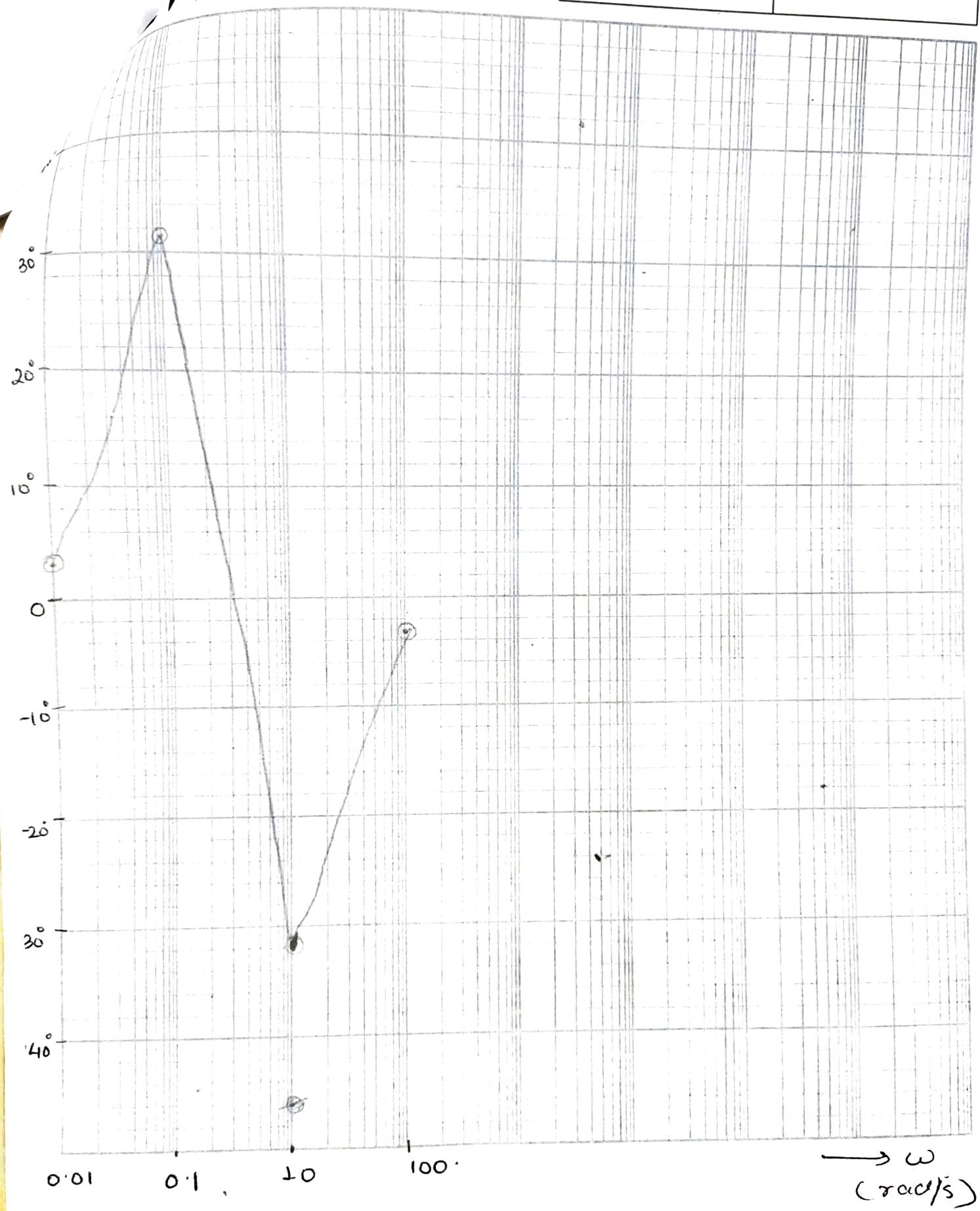

Quiz 4 - Set 2 Solutions

Set-2

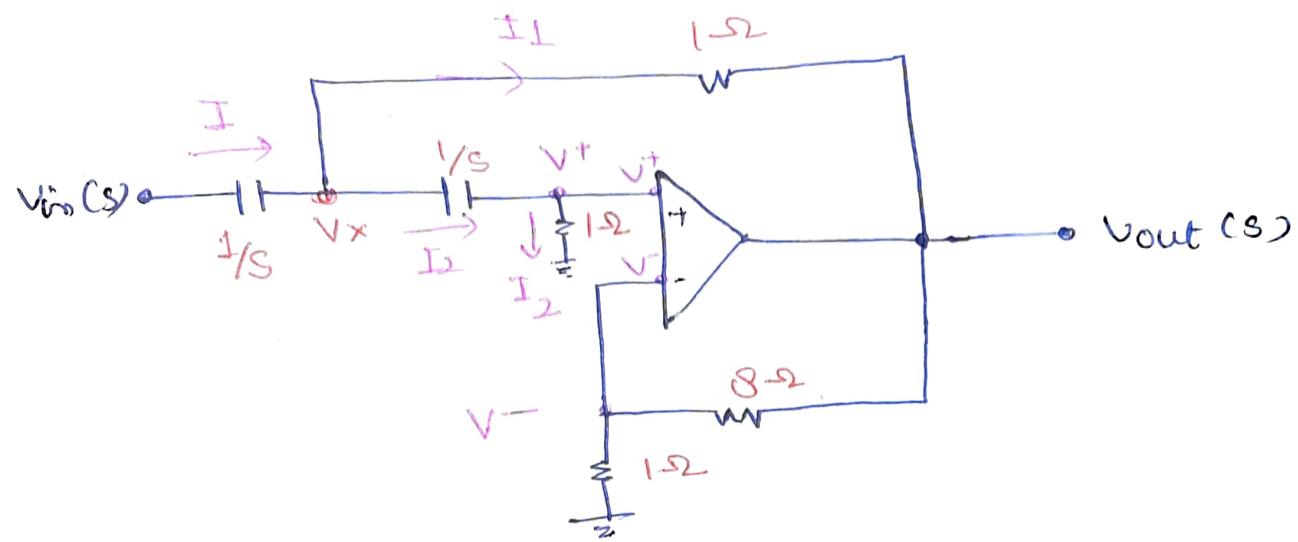

∴ it is an ideal op-amp.

∴ we can write,

$$V^- = V_+ = V_{out} \left(\frac{1}{s} \right) = \frac{V_{out}}{s} \quad \text{--- (1)}$$

$$\text{Now, } I_2 = \frac{V_u - V^+}{1/s} = \frac{V^+ - 0}{1}.$$

$$\Rightarrow sV_u = V_0 + sV^+ \quad \text{--- (2)}$$

$$\Rightarrow V_u = \frac{V^+ (1+s)}{s}$$

Applying KCL at V_n .

$$\frac{V_{in} - V_n}{1/s} = \frac{V_n}{1/s + 1} + \frac{V_n - V_{out}}{1}.$$

$$\Rightarrow s(V_{in} - V_n) = \frac{sV_n}{s+1} + V_n - V_{out}.$$

$$= V_n \left[\frac{s}{s+1} + 1 \right] - V_{out}.$$

$$\Rightarrow s(V_{in} - V_n) = V_n \left[\frac{2s+1}{s+1} \right] - V_{out}.$$

$$\Rightarrow sV_{in} = V_n \left[\frac{2s+1}{s+1} + s \right] - V_{out}.$$

$$\Rightarrow sV_{in} = V_n \left[\frac{as+1+s(s+1)}{(s+1)} \right] - V_{out}.$$

$$\Rightarrow sV_{in} = V_n \left[\frac{s^2+3s+1}{s+1} \right] - V_{out}.$$

$$\Rightarrow sV_{in} = \left(\cancel{\frac{s+1}{s}} \right) V^+ \left[\frac{s^2+3s+1}{s+1} \right] - V_{out}.$$

$$\Rightarrow sV_{in} = \left[\frac{s^2+3s+1}{s} \right] \frac{V_{out} - V_{out}}{g}.$$

$$\Rightarrow V_{in} = \frac{V_{out}}{g} \left[\frac{s^2+3s+1-gs}{gs} \right]$$

$$\Rightarrow V_{\text{in}} = V_{\text{out}} \left[\frac{s^2 - 6s + 1}{9s^2} \right]$$

$$\Rightarrow \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{9s^2}{s^2 - 6s + 1}$$

$$\therefore H(s) = \frac{9s^2}{s^2 - 6s + 1}$$

Replacing s by $j\omega$,

$$H(\omega) = \frac{9\omega^2}{-\omega^2 - j6\omega + 1} = \frac{9\omega^2}{\omega^2 - 1 + j6\omega}$$

$$\text{Now, } |H(\omega)| = \frac{9\omega^2}{\sqrt{(\omega^2 - 1)^2 + 36\omega^2}} \xrightarrow{\text{to dB}} 20 \log_{10} \left(\frac{9\omega^2}{\sqrt{(\omega^2 - 1)^2 + 36\omega^2}} \right) + 36 \text{ dB}$$

$$\angle H(j\omega) = -\tan^{-1} \left[\frac{6\omega}{\omega^2 - 1} \right]$$

$$\text{Poles of } \omega = \omega_1 = 5.82 \text{ rad/s}$$

$$\omega_2 = 0.17 \text{ rad/s}$$

ω	$ H(\omega) \text{ dB}$	$\angle H(\omega)$
0.01	-60.89	3.43°
0.17	-18.9	31.22°
0.1	-0.10	46.4°
5.82	18.70	-46.73°
20	28.40	-31.22°
100.	43.40	-3.43°


From the observations in the plot & transfer function obtained, we can say that the given filter is -

- 1) Active filter
- 2) High pass filter.
- 3) Second order filter.

Magnitude Plot $|H(\omega)|$

EEWeb


TITLE	
NAME	DATE

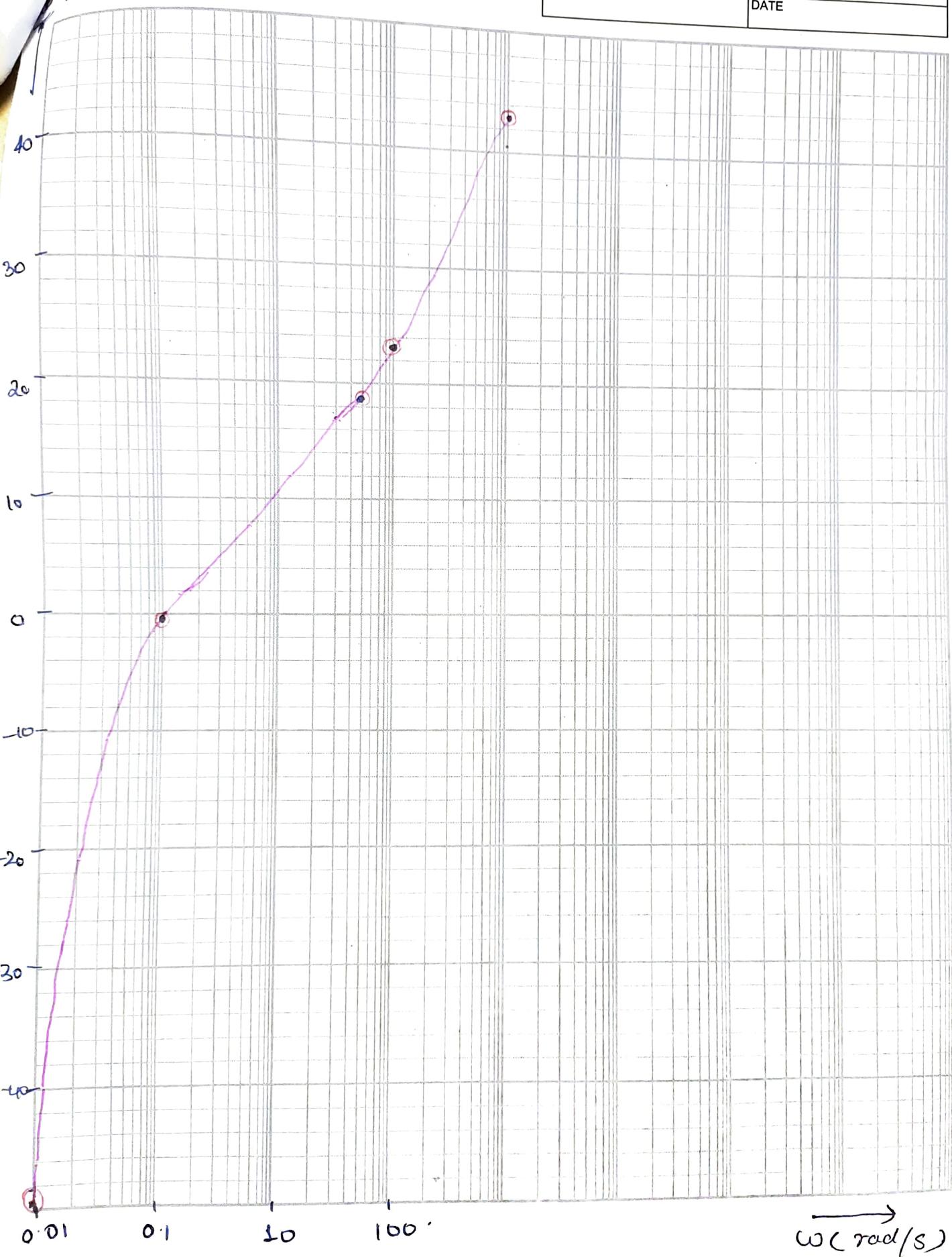


EEWeb

Phase plot
 $\angle H(\omega)$

TITLE	
NAME	DATE

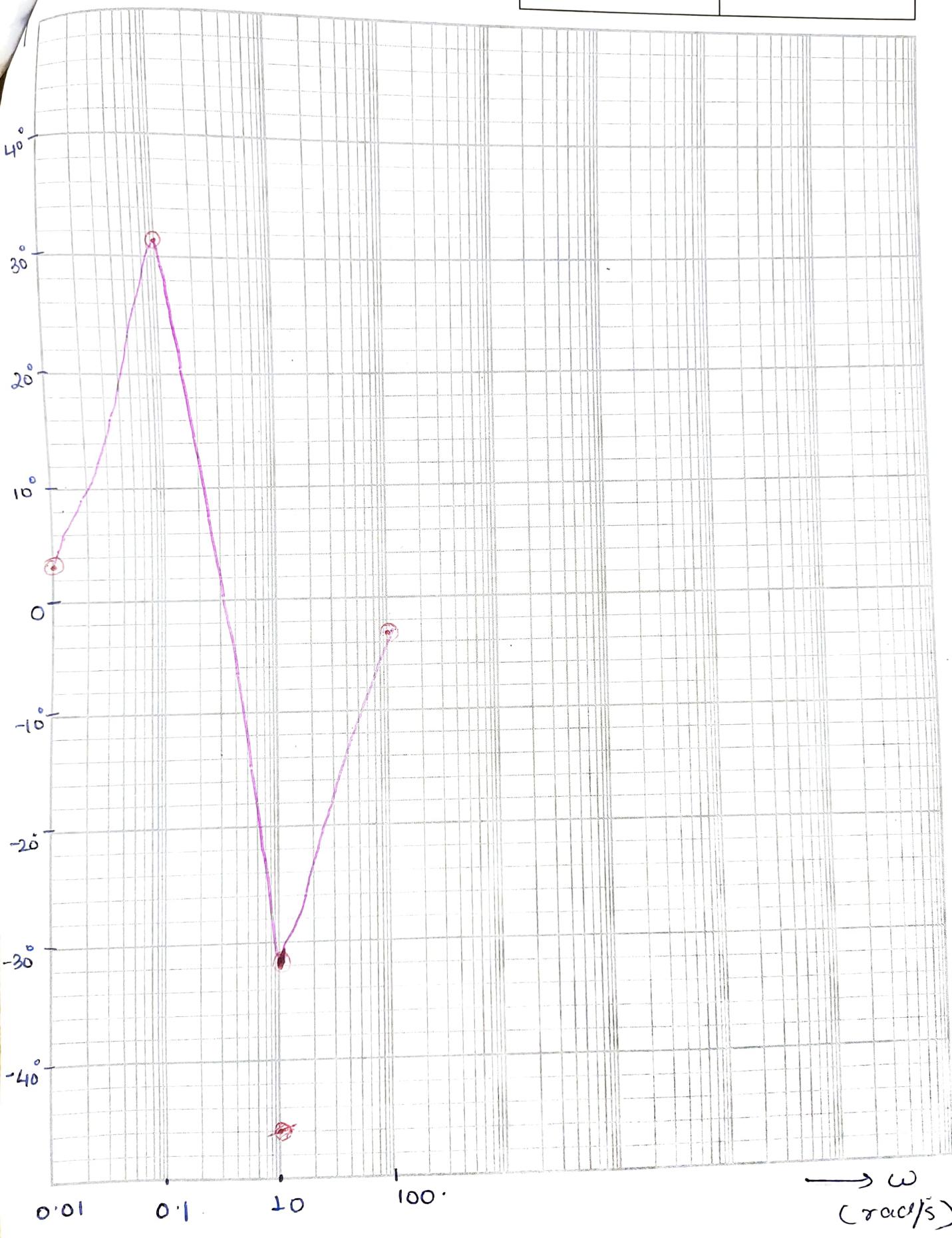

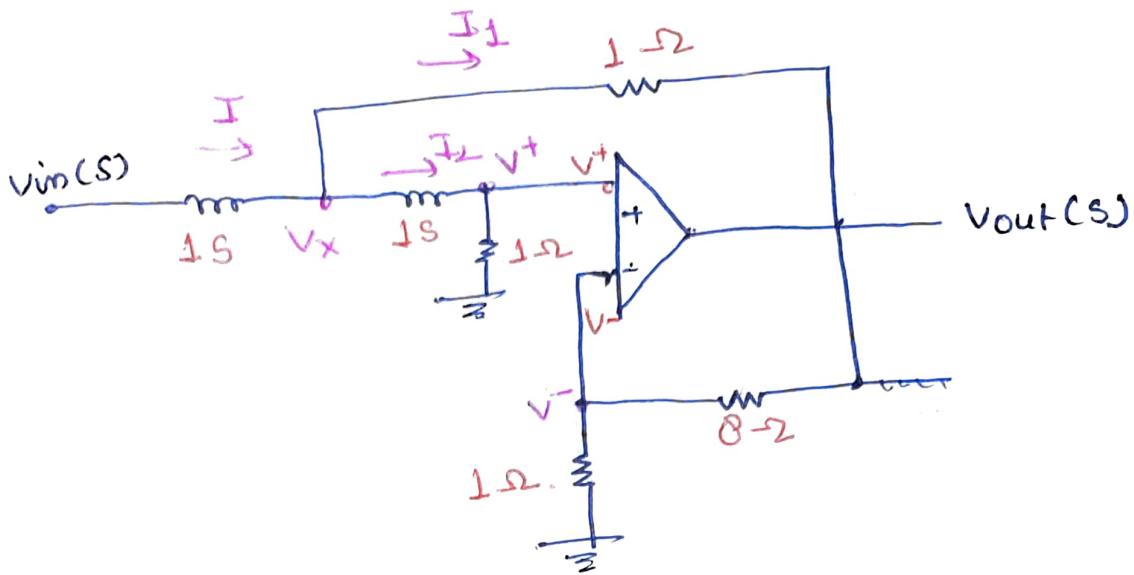

\therefore it is an ideal op-amp.

\therefore we can write,

$$V^- = V^+ = V_{out} \left(\frac{1}{g} \right) = \frac{V_{out}}{g} \quad \text{--- (1)}$$

bz.

$$\text{Now, } I_2 = \frac{V_n - V^+}{s} = \frac{V^+ - 0}{1}$$

$$\Rightarrow V_n - V^+ = sV^+$$

$$\Rightarrow V_n = (1 + s)V^+ \quad \text{--- (2)}$$

Now applying KCL,

$$I = I_1 + I_2.$$

$$\Rightarrow \frac{V_{in} - V_n}{s} = \frac{V_n - V_{out}}{s} + \frac{V_n}{(1+s)}$$

$$\Rightarrow \frac{V_{in} - V_n}{s} = V_n - V_{out} + \frac{V_n}{1+s}.$$

$$\Rightarrow \frac{V_{in}}{s} = V_n \left[\frac{1}{s} + 1 + \frac{1}{s+1} \right] - V_{out}.$$

$$\Rightarrow \frac{V_{in}}{s} = V_n \left(\frac{1+s}{s} + \frac{1}{s+1} \right) - V_{out}$$

$$\Rightarrow \frac{V_{in}}{s} = V_n \left[\frac{(s+1)^2 + s}{s(s+1)} \right] - V_{out}$$

from ②

$$\Rightarrow \frac{V_{in}}{s} = (1+s)V^+ \left[\frac{(s+1)^2 + s}{s(s+1)} \right] - V_{out}.$$

from ①

$$\Rightarrow \frac{V_{in}}{s} = (1+s) \left[\frac{(s+1)^2 + s}{s(s+1)} \right] \frac{V_{out} - V_{out}}{g} - V_{out}$$

$$\Rightarrow \frac{V_{in}}{s} = V_{out} \left[\frac{(s+1)^2 + s - g}{gs} \right]$$

$$\Rightarrow \frac{V_{in}}{s} = V_{out} \left[\frac{(s+1)^2 + s - gs}{ggs} \right]$$

$$\Rightarrow \frac{V_{in}}{V_{out}} = \frac{(s+1)^2 - 8s}{9}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{9}{(s+1)^2 - 8s} = \frac{9}{s^2 - 6s + 1}$$

$$\therefore H(s) = \frac{9}{s^2 - 6s + 1}$$

Now, we can write,

$$H(s) = \frac{9}{(s - 5.82)(s - 0.17)}$$

$$\Rightarrow H(j\omega) = \frac{9}{(j\omega - 5.82)(j\omega - 0.17)}$$

$$\therefore \text{Poles} \rightarrow \omega_1 = 5.82 \text{ rad/s}$$

$$\omega_2 = 0.17 \text{ rad/s.}$$

$$\text{Now } |H(\omega)| = \frac{9}{\sqrt{1-\omega^2 + 36\omega^2}} \xrightarrow{\text{indB}} 20 \log_{10} \left(\frac{9}{\sqrt{1-\omega^2 + 36\omega^2}} \right) \text{ dB.}$$

$$\angle H(\omega) = -\tan^{-1} \left[\frac{6\omega}{1-\omega^2} \right]$$

ω	$ H(\omega) \text{ dB}$	$\angle H(\omega)$
0.01	19.08	3.43°
0.1	17.87	31.22°
0.17	16.16	-46.4°
5.82	-14.53	-46.73°
10	-26.35 -16.35	-31.22°
100	-36.35	-3.43°


a) we can observe and say that it is —

- ① Active filter
- ② Second order
- ③ low pass filter.

Magnitude plot.
 $|H(\omega)|$

EEWeb

TITLE	
NAME	DATE

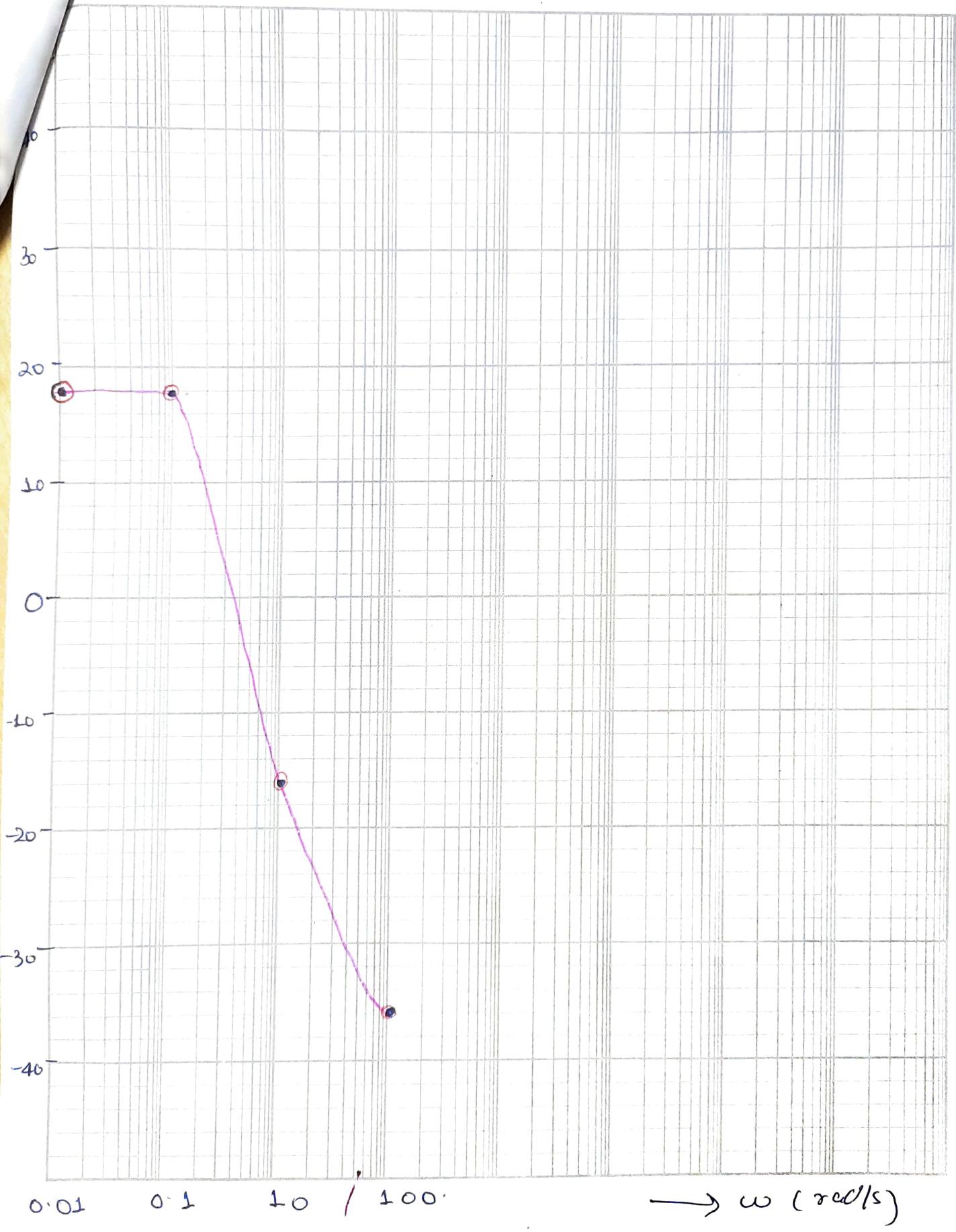

EWeb

Phase-Plot

$\angle H(\omega)$

TITLE	
NAME	DATE

