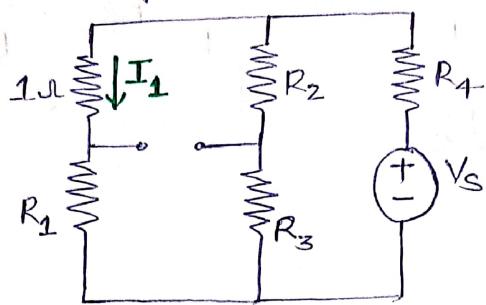


ASSIGNMENT-2 RUBRIC


SOL(1) $\frac{1}{2}$

Case(I) : When Voltage Source (V_S) is acting alone



$\rightarrow (0.5 \text{ Points})$

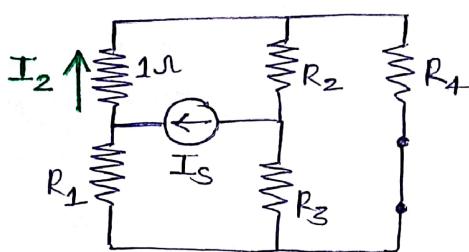Case(II) : When current source (I_S) is acting alone



$\rightarrow (0.5 \text{ Points})$

\therefore Current through '1Ω' resistance, $I = (\pm I_1 \mp I_2)$ — ①
(By using Superposition Theorem) $\rightarrow (1 \text{ Points})$

as we know that — $P = I^2 \cdot R$

$$I = \sqrt{(P/R)} \quad \text{— ②}$$

By eqⁿ ① & eqⁿ ②, we get —

$$\sqrt{(P/R)} = \pm \sqrt{(P_1/R)} \mp \sqrt{(P_2/R)}$$

$$\sqrt{P} = \pm \sqrt{P_1} \mp \sqrt{P_2} \quad (\because R = 1\Omega)$$

$$P = (\pm \sqrt{P_1} \mp \sqrt{P_2})^2 \quad \text{— ③} \quad \rightarrow (2 \text{ Points})$$


\therefore Total power dissipation in 1Ω resistance,

$$P = (\sqrt{576} - \sqrt{1})^2$$

$$P = 529 \text{ W}$$

$\rightarrow (1 \text{ Points})$

SOL(2)

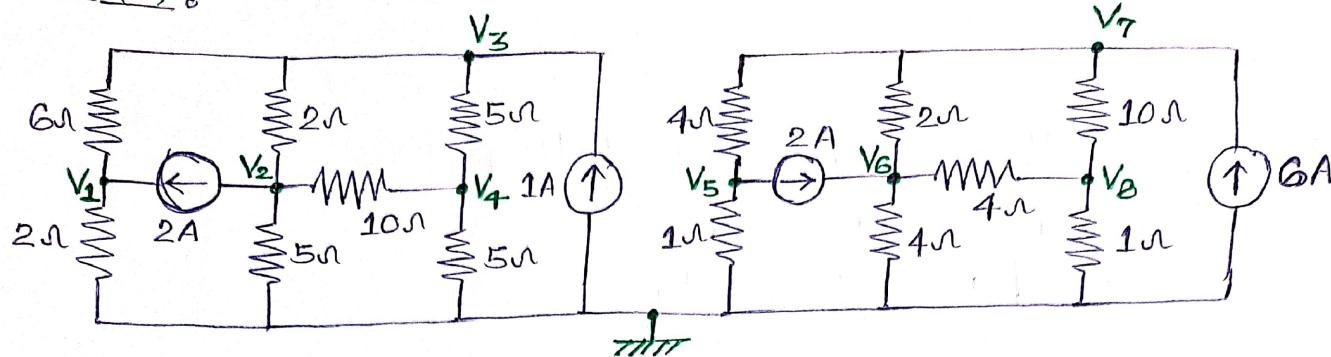

at Node ①—

$$\frac{V_1}{2} + \frac{V_1 - V_3}{6} = 2$$

$$4V_1 - V_3 = 12 \quad \text{--- } ①$$

→ (0.5 Points)

at Node ②—

$$\frac{V_2}{5} + \frac{V_2 - V_3}{2} + \frac{V_2 - V_4}{10} + 2 = 0$$

$$8V_2 - 5V_3 - V_4 = (-20) \quad \text{--- } ②$$

→ (0.5 Points)

at Node ③—

$$\frac{V_3 - V_1}{6} + \frac{V_3 - V_2}{2} + \frac{V_3 - V_4}{5} = 1$$

$$-5V_1 - 15V_2 + 26V_3 - 6V_4 = 30 \quad \text{--- } ③ \quad \rightarrow (0.5 \text{ Points})$$

at Node ④—

$$\frac{V_4}{5} + \frac{V_4 - V_2}{10} + \frac{V_4 - V_3}{5} = 0$$

$$-V_2 - 2V_3 + 5V_4 = 0 \quad \text{--- } ④$$

→ (0.5 Points)

By eqn ①, ②, ③ & ④— $V_2 = (-2.35)V$, $V_3 = (0.31)V$, $V_4 = (-0.35)V$,

$$V_1 = (3.08)V$$

→ (4 × 0.125 Points)

at Node ⑤—

$$\frac{V_5}{1} + \frac{V_5 - V_7}{4} + 2 = 0$$

$$5V_5 - V_7 = (-8) \quad \text{--- } ⑤$$

→ (0.5 Points)

at Node ⑥—

$$\frac{V_6}{4} + \frac{V_6 - V_8}{4} + \frac{V_6 - V_7}{2} = 2$$

$$4V_6 - 2V_7 - V_8 = 0 \quad \text{--- } ⑥$$

→ (0.5 Points)

at Node ⑦—

$$\frac{V_7 - V_5}{4} + \frac{V_7 - V_6}{2} + \frac{V_7 - V_8}{10} = 6$$

$$-5V_5 - 10V_6 + 17V_7 - 2V_8 = 120 \quad \text{--- } ⑦$$

→ (0.5 Points)



at Node ⑧ —

$$\frac{V_8}{1} + \frac{V_8 - V_6}{4} + \frac{V_8 - V_7}{10} = 0$$

$$-5V_6 - 2V_7 + 27V_8 = 0 \quad \text{--- ⑧}$$

→ (0.5 Points)

By eqn (5), (6), (7) & (8), we get —

$$V_6 = 9.22 \text{ V}$$


$$V_7 = 13.10 \text{ V}$$

$$V_8 = 2.68 \text{ V}$$

$$V_5 = 1.02 \text{ V}$$

→ (4 × 0.125 Points)


SOL(3) :-

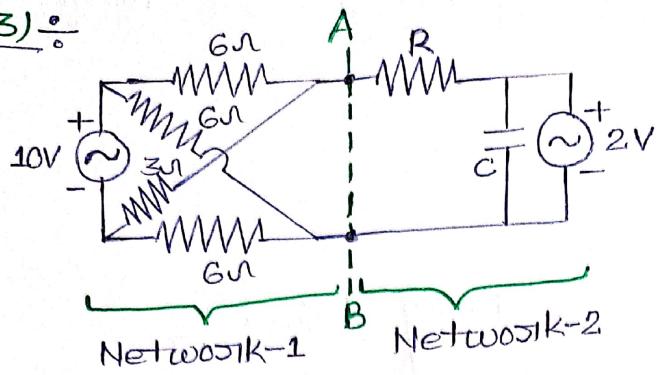

For maximum power transfer from Network-1 (work as a source) to Network-2 (work as a load), the value of equivalent resistance of Network-2 is must be equal to source internal resistance (Network-1, thevenin resistance).


Network-1 Thevenin equivalent circuit — → (0.5 Points)

Case(I) : For R_{th}

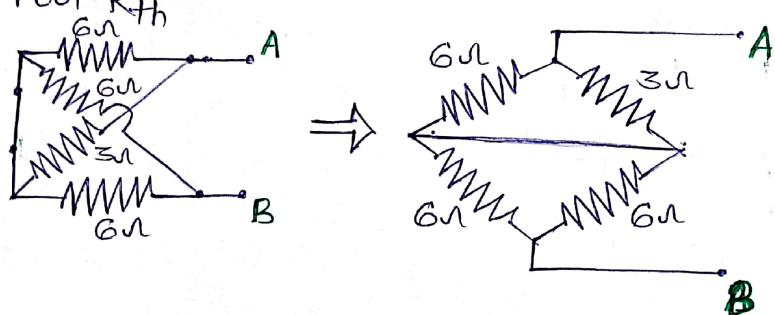


$$\therefore R_{th} = 5\Omega \quad \text{--- ①} \rightarrow (1 \text{ Points})$$

Case(II) : For V_{th}/V_{AB}

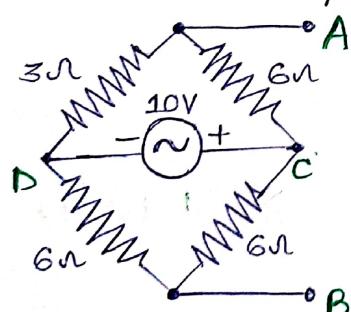


$$\begin{aligned} \therefore V_{th} &= V_{AB} = (V_A - V_B) = \left(\frac{3}{9} \times 10\right) - \left(\frac{6}{12} \times 10\right) \\ &= \left(-\frac{5}{3}\right) \text{ volt} \quad \text{--- ②} \rightarrow (1 \text{ Points}) \end{aligned}$$

Now reduced circuit —

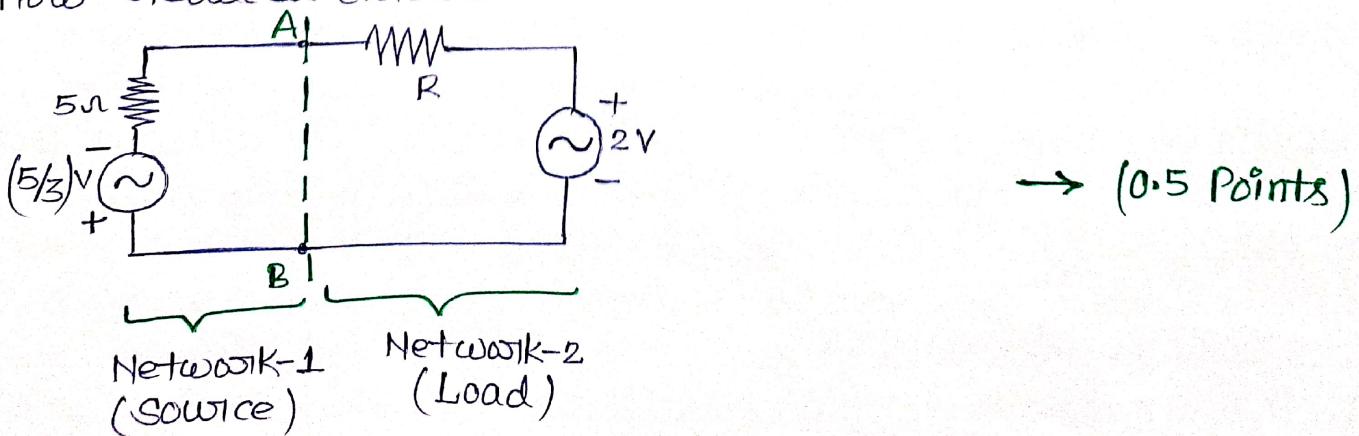

→ (0.5 Points)

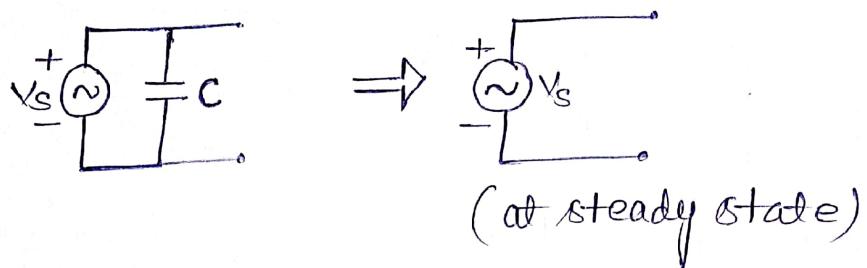
as we know, at steady state capacitor work as an open circuit.



Equivalent resistance of load (Network K-2) = $R_{th} = 5\Omega$

(for max^m power)

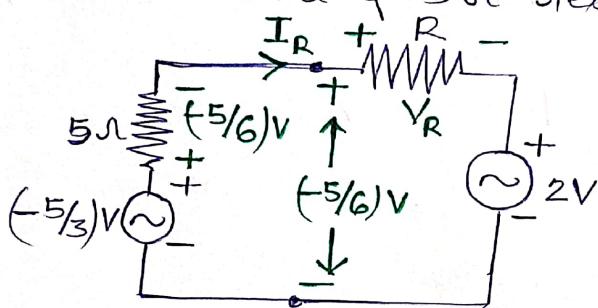Hence source voltage $\left[-\frac{5}{3}\right]V$ will be equally distributed across load & 5Ω resistance ie $\left[-\frac{5}{6}\right]V$. (transfer)



→ (1 Point)

∴ Voltage across ' R ' = $V_R = \left(-\frac{5}{6}\right) V$


∴ Current through ' R ' = $I_R = \frac{\left(-\frac{5}{6}\right)}{5} = \left(-\frac{1}{6}\right) A$

∴ Value of Resistor ' R ' = $\left(\frac{V_R}{I_R}\right)$

$$= (17) \Omega$$

→ (1 Point)


SOL(4):

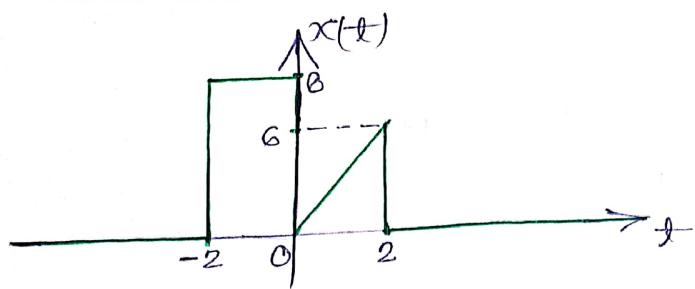

$$i(t) = \frac{d}{dt}[x(t)] = \text{slope of } x(t) \text{ w.r.t. } t \cdot t^6$$

[in ampere]

→ (3 Points)

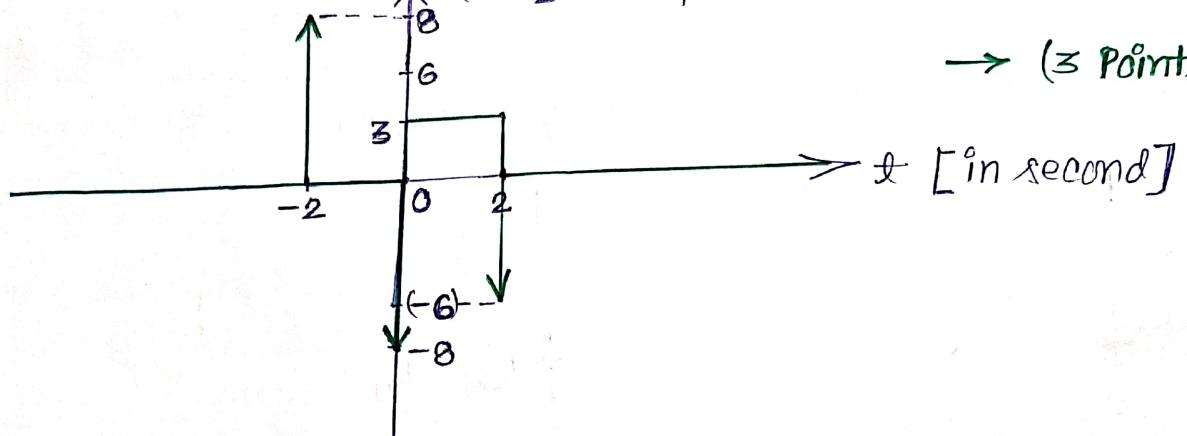

∴ Charge acquired by capacitor after 2 second,

$$Q = \int_{-2}^2 i(t) \cdot dt = \text{area of } i(t) \text{ w.r.t. } t^6 \quad [-2 \leq t \leq 2]$$


$$Q = 0 - 0 + 2 \times 3 - 6$$

$$\therefore Q = 0 \text{ Coulomb}$$

→ (2 Points)

SOL(5)


Case(I): To get R_N (Norton Resistance)

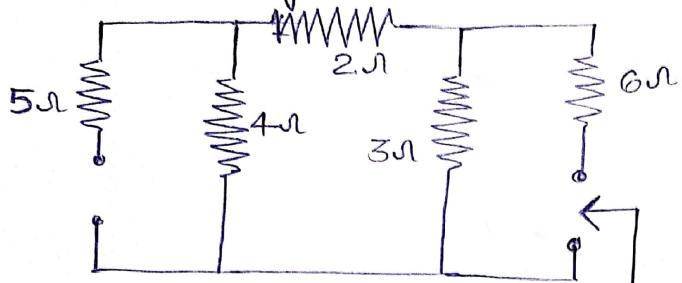

$$R_N = 6 + \frac{3 \times 6}{3+6} = 8\Omega \quad \text{--- ①}$$

→ (2 Points)

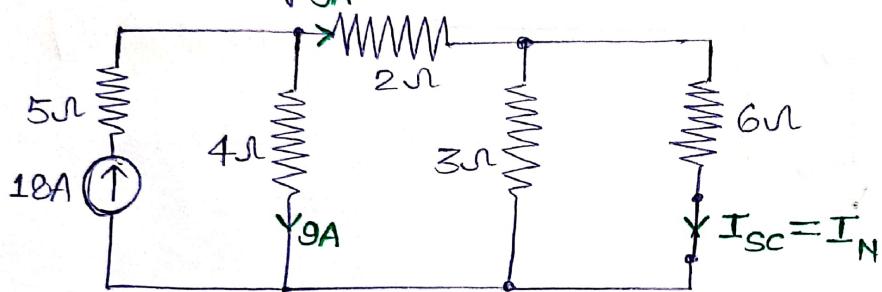
Case(II): To get I_N/I_{SC} (Norton Current)



$$\therefore I_{SC} = I_N = \frac{3}{3+6} \times 9 = 3A \quad \text{--- ②}$$

→ (2 Points)

Now reduced circuit diagram —


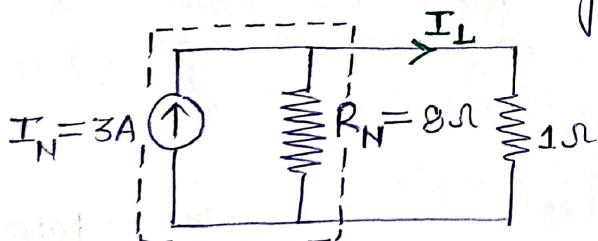


$$\therefore \text{Current in } 1\Omega \text{ resistance} = I_L = \left(\frac{8}{8+1}\right)3$$

$$= \left(\frac{8}{9}\right)A$$

→ (1 Points)

SOL(6)

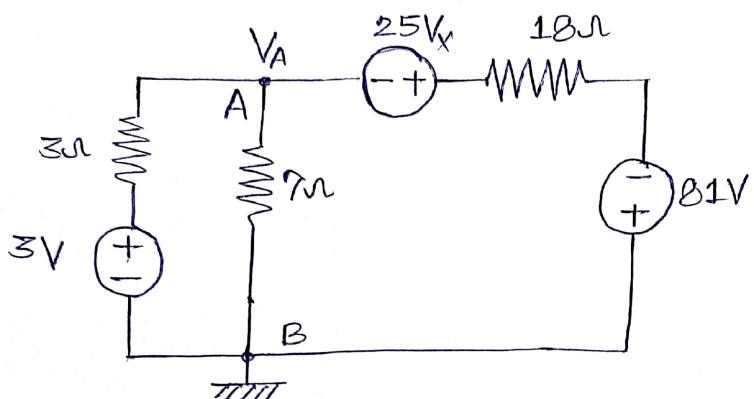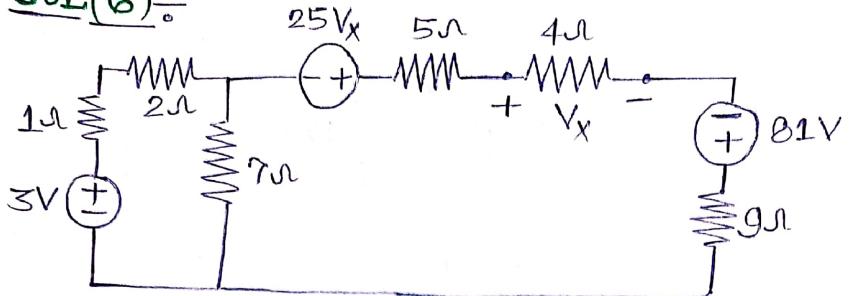

→ (1 Points)

By using Nodal analysis (at node A),

$$\left(\frac{V_A - 3}{3}\right) + \left(\frac{V_A}{7}\right) + \left(\frac{V_A + 25V_x + 81}{18}\right) = 0$$

$$67V_A + 175V_x = (-441) \quad \text{--- } ①$$

→ (1.5 Points)

By circuit diagram—

$$\left(\frac{V_A + 25V_x + 81}{18}\right) = \left(\frac{V_x}{4}\right)$$

$$4V_A + 82V_x = (-324) \quad \text{--- } ②$$


→ (1.5 Points)

By solving eqn ① & ②, we get—


$$\therefore V_x = (-4.16) \text{ Volt}$$

→ (1 Points)


SOL(7)

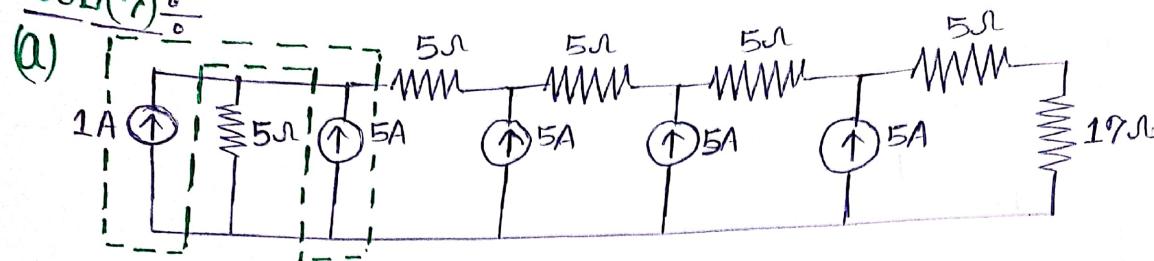


(0.25 Points)

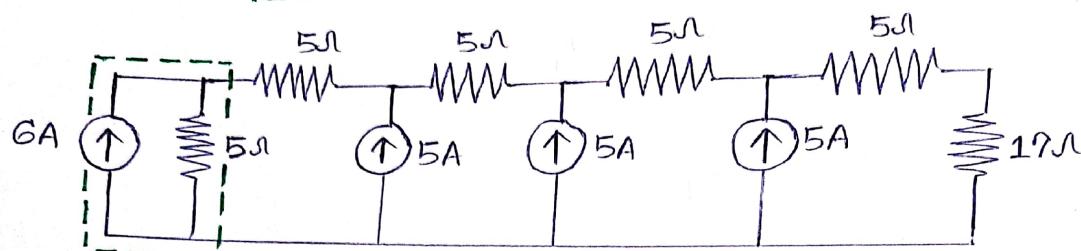


(0.25 Points)

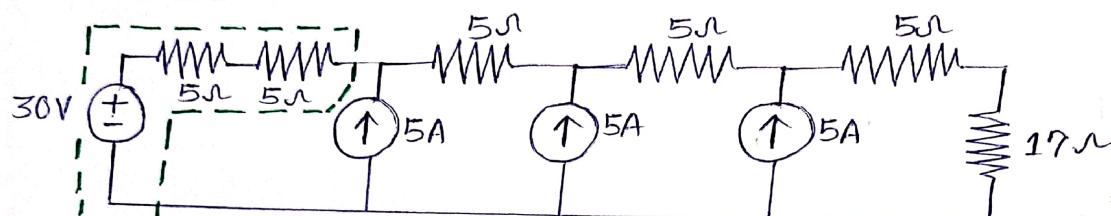


(0.25 Points)

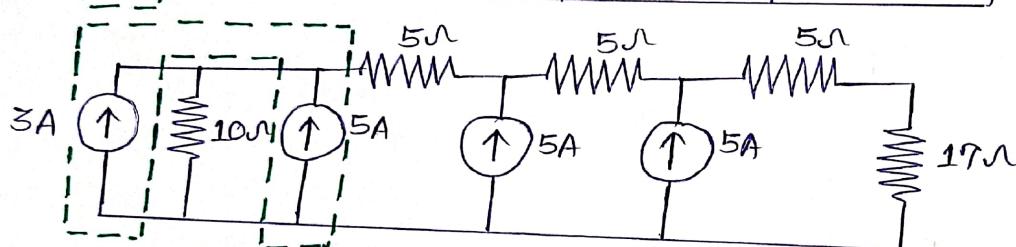


(0.25 Points)

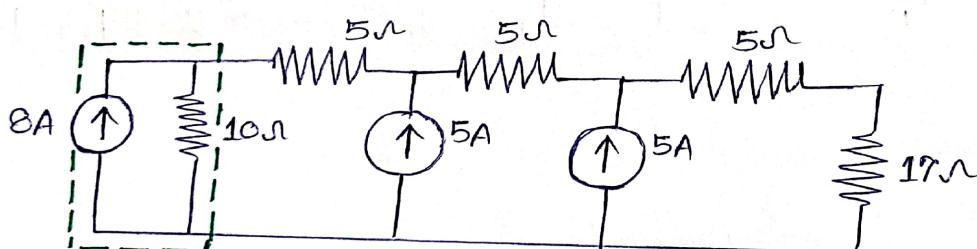


(0.25 Points)

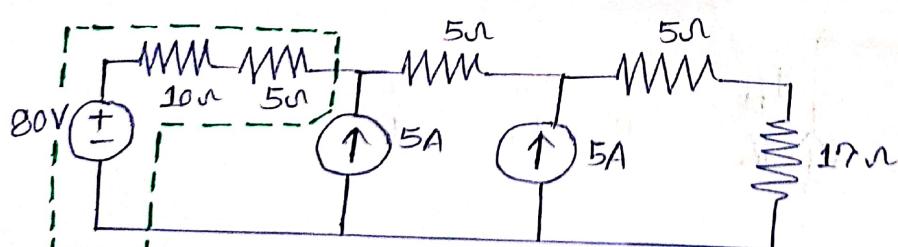


(0.25 Points)

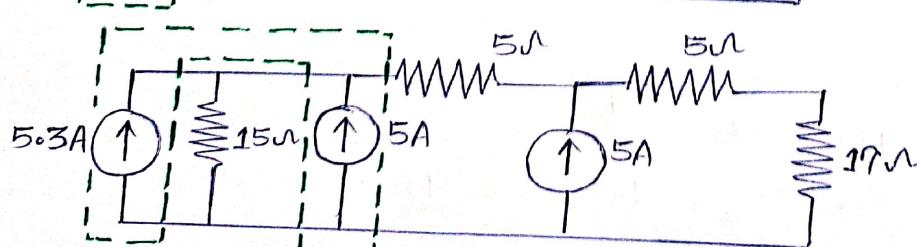


(0.25 Points)

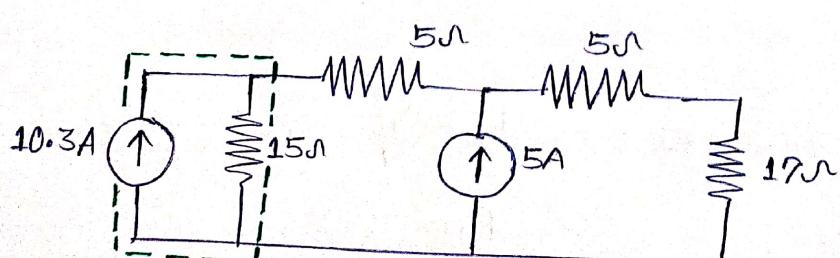


(0.25 Points)

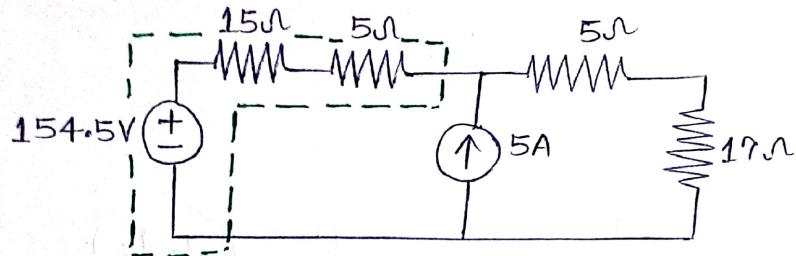


(0.25 Points)

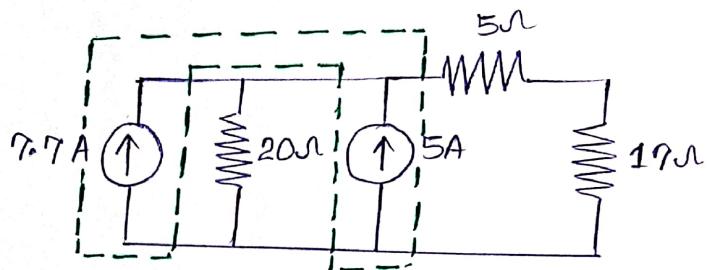


(0.25 Points)

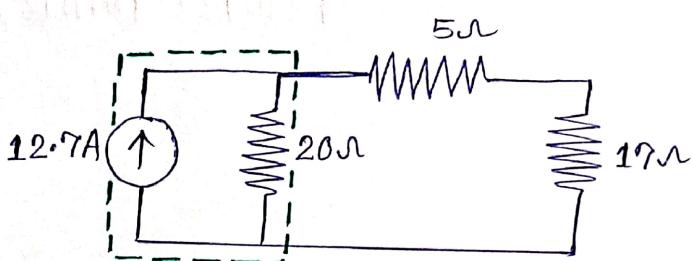

(0.25 Points)

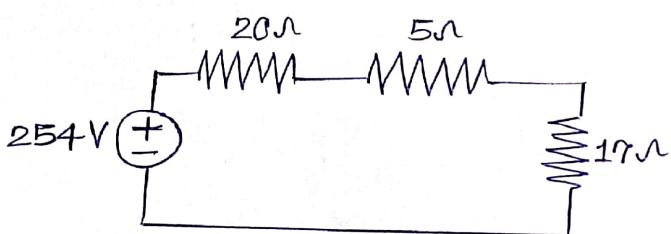

(0.25 Points)

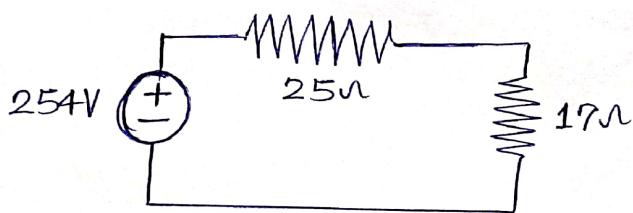




(1.25 Points)

$$(6) \text{ Power dissipated by } 17\Omega \text{ resistor} = \left(\frac{254}{25+17} \right)^2 \times 17 \\ = 621.75 \text{ Watt}$$

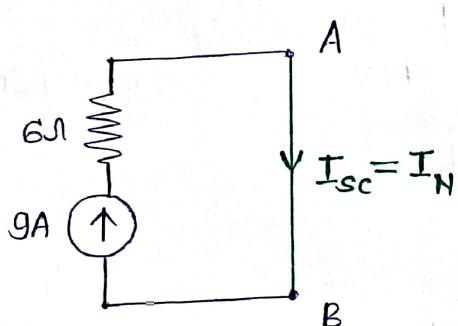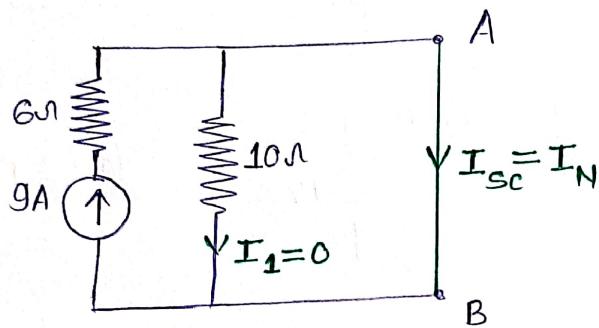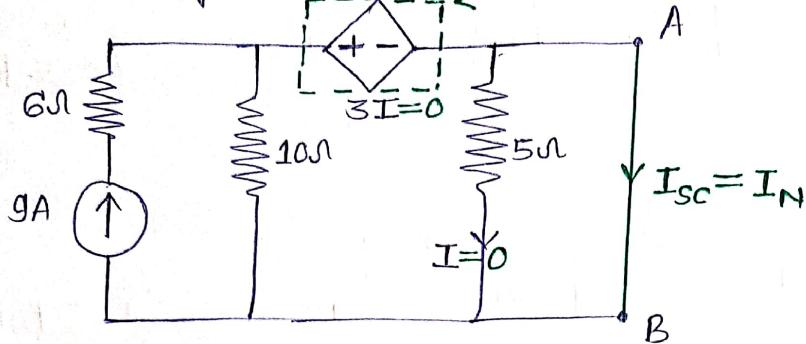(0.75 Points)


SOL(B)

Case(I): To get I_N (I_{SC}) short circuit



$$\therefore I_{SC} = I_N = 9A \rightarrow (2.5 \text{ Points})$$

Case(II): To get R_N Supernode

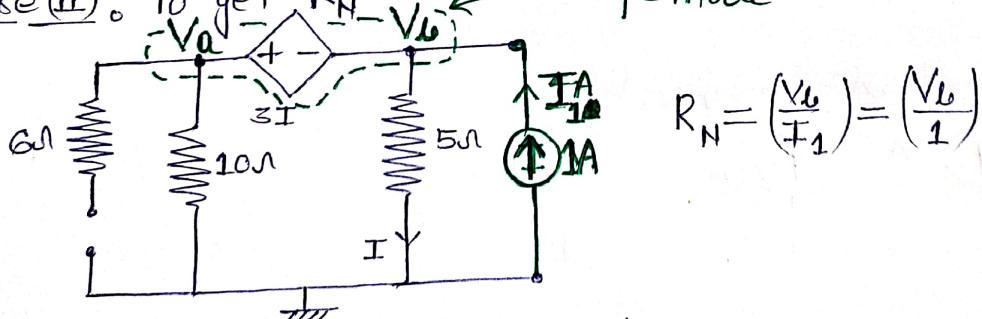

$$R_N = \left(\frac{V_b}{I} \right) = \left(\frac{V_b}{1} \right)$$

KCL at Supernode — $\frac{V_a}{10} + \frac{V_b}{5} = 1$

$$V_a + 2V_b = 10 \quad \text{--- } ①$$

$$V_a - V_b = 3I \quad \text{--- } ②$$

$$(V_b/5) = I \quad \text{--- } ③$$

By using eqn ①, ② & ③, we get — $R_N = \frac{V_b}{1} = \frac{50}{18} = 2.8\Omega$

$$\therefore R_N = 2.8\Omega$$

$$\rightarrow (2.5 \text{ Points})$$