


End-Sem Examination_Solutions


ECE 113 Basic Electronics

Maximum Marks: 60

Q1 (a).

[5 Marks]

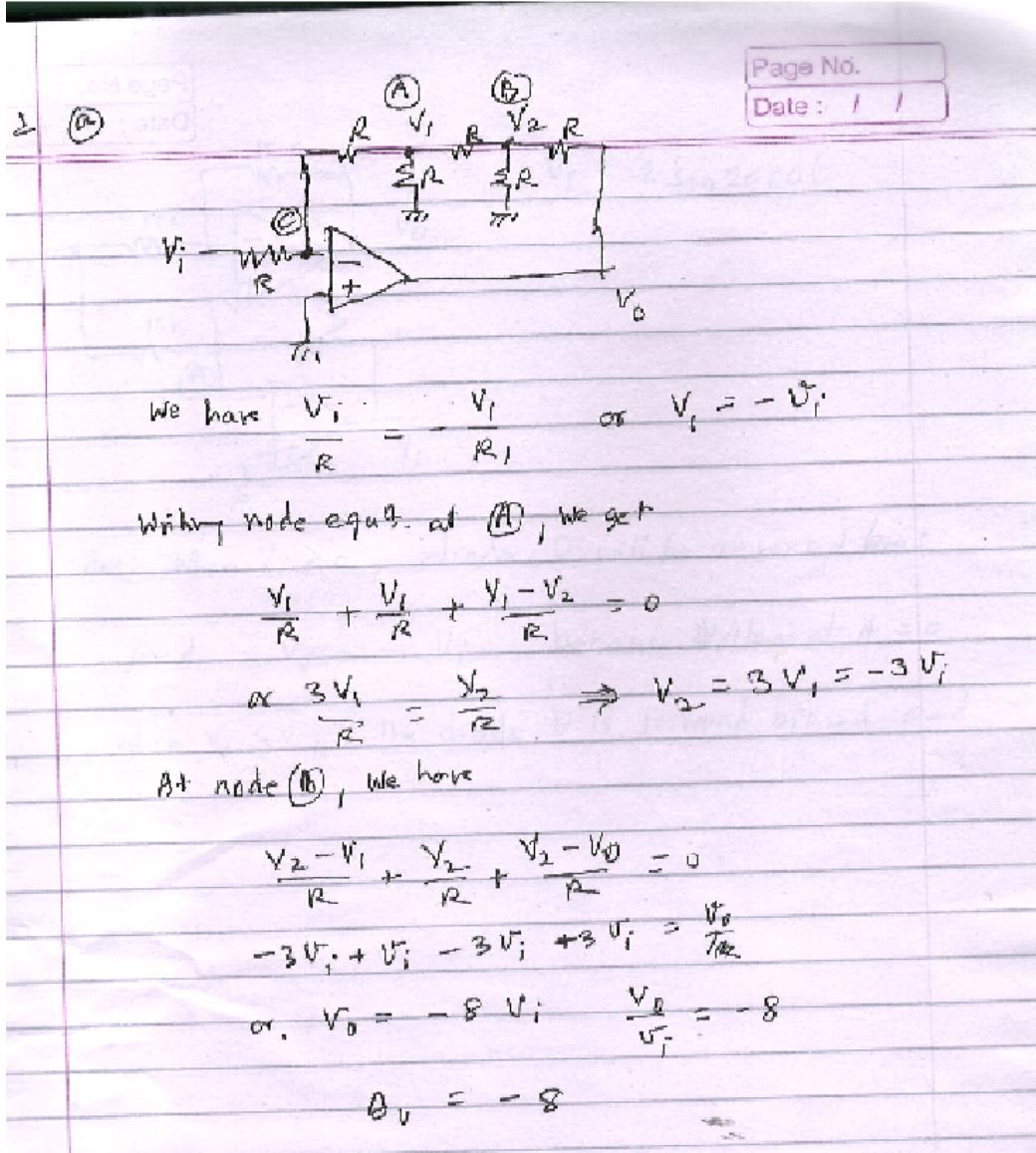

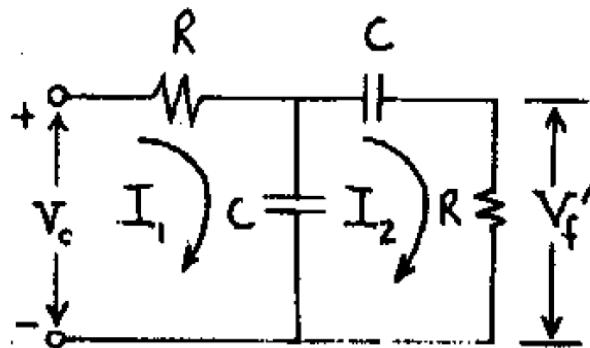

$$(a) \text{ Let } X = \frac{1}{\omega C}. \quad \text{Then}$$

$$V_o = I_1(R - jX) - I_2(-jX)$$

$$0 = -I_1(-jX) + I_2(R - j2X)$$


$$I_1 = \left(\frac{R - j2X}{-jX}\right) I_2 = \left(2 + j\frac{R}{X}\right) I_2$$

$$\therefore V_o = I_2 \left[(R - jX) \left(2 + j\frac{R}{X}\right) + jX \right] = I_2 \left[3R + j\left(\frac{R^2}{X} - X\right) \right]$$

$$\frac{V_f}{V_o} = \frac{I_2 R}{V_o} = \frac{R}{3R + j\left(\frac{R^2}{X} - X\right)} = \frac{1}{3 + j\left(\frac{R}{X} - \frac{X}{R}\right)} = \frac{1}{3 + j(\omega RC - \frac{1}{\omega RC})}$$

2 @

Date: / /

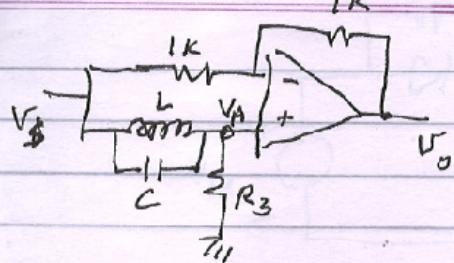

$$\text{Z} = \frac{j\omega L \times \frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C}} = \frac{j\omega CL}{1 - \omega^2 LC}$$

$$V_A = \frac{R_3}{R_3 + Z} \cdot V_s$$

$$= \frac{R_3}{R_3 + \frac{j\omega LC}{1 - \omega^2 LC}} \cdot \frac{V_s}{R_3(1 - \omega^2 LC) + j\omega LC}$$



$$\frac{V_o}{V_s} = -V_s + ZV_A \\ = -V_s + \frac{2R_3(1 - \omega^2 LC) V_s}{R_3(1 - \omega^2 LC) + j\omega LC}$$

$$= V_s \left[\frac{-R_3(1 - \omega^2 L) - j\omega LC}{R_3(1 - \omega^2 LC) + j\omega LC} \right]$$

$$= V_s \left[\frac{R_3(1 - \omega^2 LC) - j\omega LC}{R_3(1 - \omega^2 LC) + j\omega LC} \right]$$

$$\frac{V_o}{V_s} = \frac{R_3(1 - \omega^2 LC) - j\omega LC}{R_3(1 - \omega^2 LC) + j\omega LC}$$

2 (b)

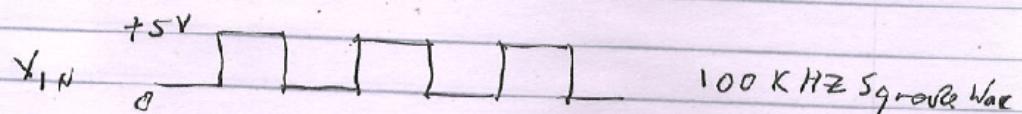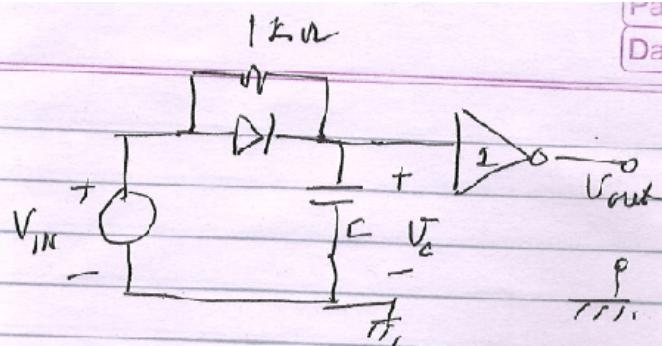

- (a) When $V_{in} = 0$, diode is not conducting, and output $V_c = 0 \text{ V}$. This gives $V_{out} = 0 \text{ V}$
- (b) When $V_{in} = +5 \text{ V}$, the diode conducts and capacitor changes to $+5 \text{ V}$ and $V_{out} = +5 \text{ V}$
- (c) When $V_{in} = 0$, the capacitor C discharges through resistance of $1\text{k}\Omega$ and time $t = RC$

$$V_c(t) = 5 e^{-t/RC} \text{ V}$$



$$\text{where } RC = 1\text{k} \times 2 \times 10^{-9} = 2 \times 10^{-6} \text{ sec.}$$

$$\text{Period of square wave} = \frac{1}{100 \times 10^3} = 10 \mu\text{sec.}$$

~~Want t' when $V_c(t) = 0.5$~~


$$V_c(t) \text{ discharging to } 2.5 \text{ V at } t' = \log 2 \text{ sec.}$$

Waveform will be given as

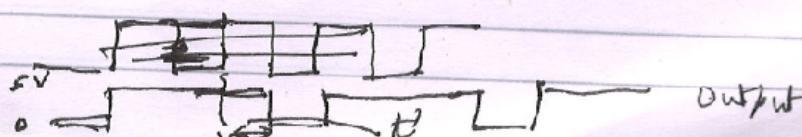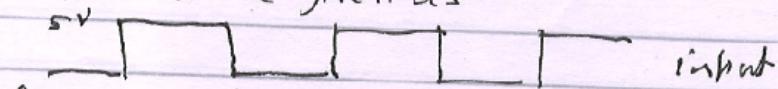

Q3 (a)


[5 Marks]

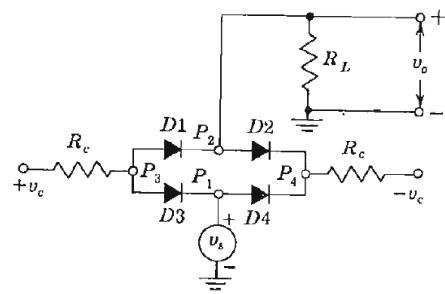

In this figure all four diodes will be conducting as long as the control signal is positive (v_c - ($-v_c$) is positive and greater than zero Volt. Under this condition Point P_1 and P_3 will be at the same potential and output will follow the input voltage.

The diodes will be reverse biased when control signal is zero. The point P_3 will be at ground potential.

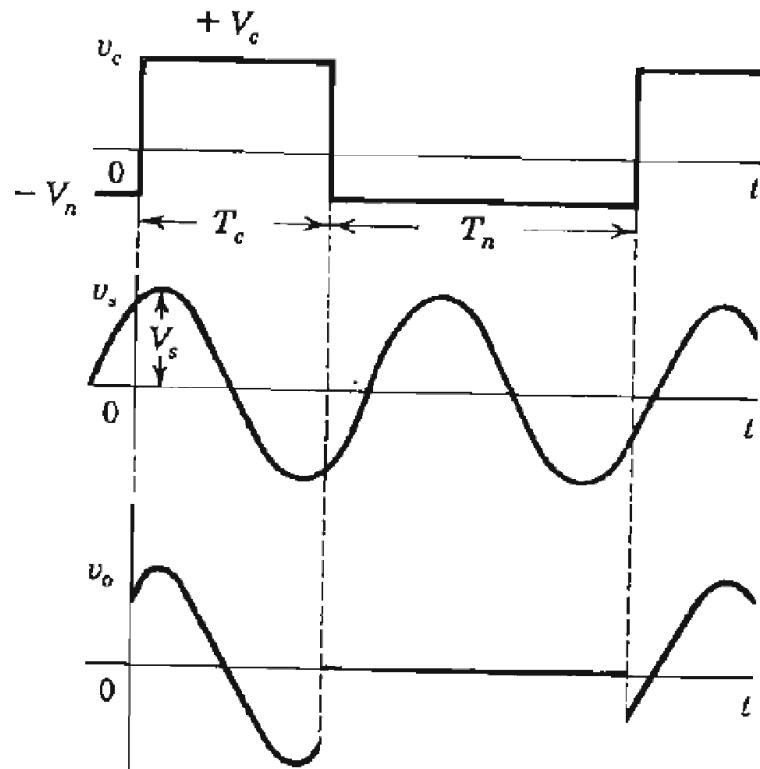Thus the output waveform will be as shown in following figure.




Q. 3 b

The required network is a ~~simple~~ simple resistance divider such that when the light is ON, the current through bulb voltage is 1.5 V and it draws 0.5 A of currents.

$$\text{So, The resistance of bulb} = \frac{1.5 \text{ V}}{0.5 \text{ A}} = 3 \Omega = R_B$$

(B) When the Bulb is off, the voltage is 2 V.

The network will be following.

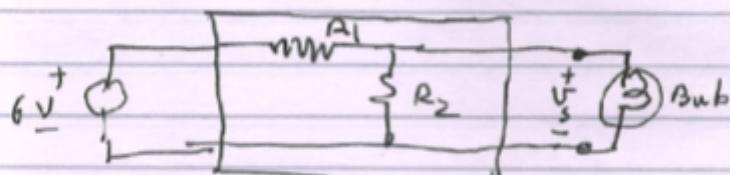

$$\text{Open circuit voltage } V_s = 2 \text{ V}$$

$$\text{When load i.e. Bulb is ON, } V_s = 1.5 \text{ V}$$

$$\text{Thus } \frac{R_2}{R_1 + R_2} \times 6 \text{ V} = 2 \text{ V} \quad \text{--- (1)}$$



$$\text{and } \frac{R_2 \parallel R_B \times 6 \text{ V}}{R_1 + (R_2 \parallel R_B)} = 1.5 \text{ V} \quad \text{--- (2)}$$

So, we get for R_1 & R_2 from eqn. (1) & (2), we


$$\text{obtain } R_1 = 3 \Omega$$

$$R_2 = 1.5 \Omega$$

4(a)

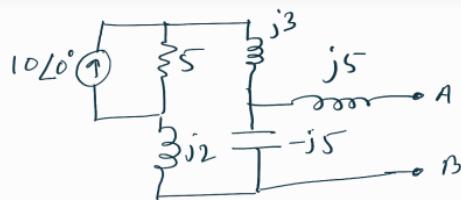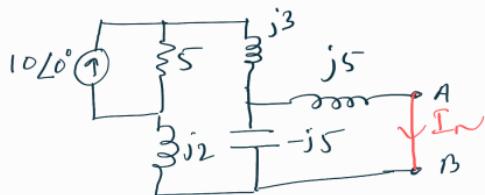For I_N 

By source transformation,

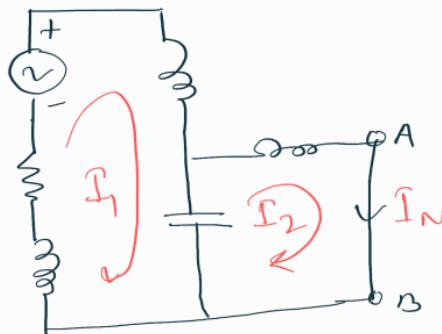


writing KVL in matrix form.

$$\begin{bmatrix} 5 & j5 \\ j5 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 10\angle0^\circ \\ 0 \end{bmatrix}$$

By Cramer's rule,

$$I_2 = \frac{\begin{vmatrix} 5 & 10\angle0^\circ \\ j5 & 0 \end{vmatrix}}{\begin{vmatrix} 5 & j5 \\ j5 & 0 \end{vmatrix}} = 10\angle-90^\circ$$


$$\therefore I_N = I_2 = 10\angle-90^\circ \text{ A}$$

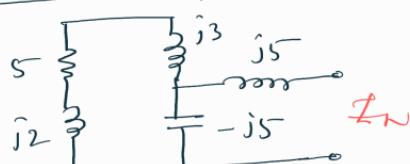Calculation of Z_N 

$$\therefore Z_N = \frac{j5 + (5+j5)(-j5)}{5 + j5 - j5}$$

$$= \underline{5\Omega}$$


So, The Norton's equivalent network is

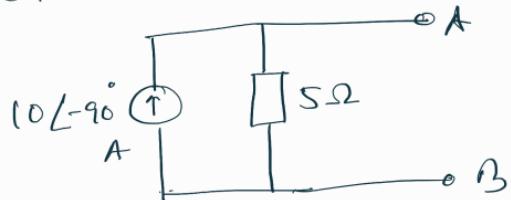


Q.4(b)

[5 Marks]

4(b)

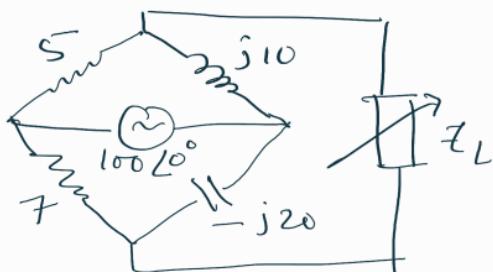

Calculation of V_{TH}

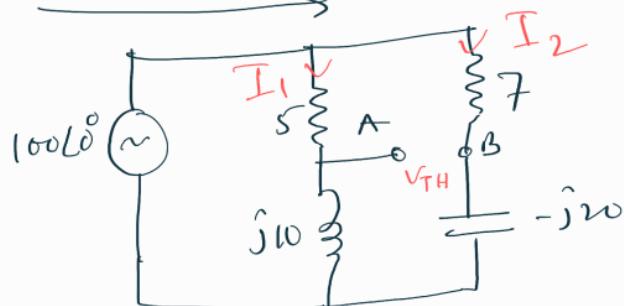


$$I_1 = \frac{100\angle 20^\circ}{5 + j10} = 8.94\angle -63.43^\circ A$$

$$I_2 = \frac{100\angle 20^\circ}{7 - j20} = 4.72\angle 70.7^\circ A$$

$$\begin{aligned}
 \text{So, } V_{TH} &= V_A - V_B \\
 &= (8.94 \angle -63.43^\circ)(j10) - \\
 &\quad (4.72 \angle 70.7^\circ)(-j20) \\
 &= 71.76 \angle 97.3^\circ \text{ V}
 \end{aligned}$$


Calculation of Z_{TH}

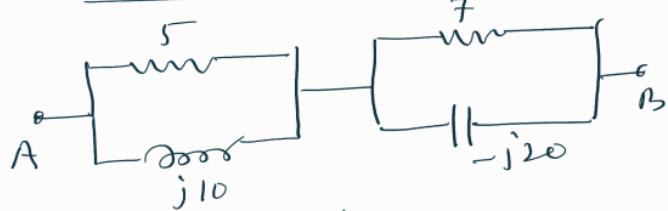

$$\begin{aligned}
 \therefore Z_{TH} &= \frac{5(j10)}{5+j10} + \frac{7(-j20)}{7-j20} \\
 &\Rightarrow \frac{50 \angle 90^\circ}{11.18 \angle 63.43^\circ} + \frac{140 \angle -90^\circ}{21.19 \angle -70.7^\circ} \\
 &\Rightarrow (10.23 - j0.18) \Omega
 \end{aligned}$$

for maximum power transfer,
the load impedance should be
complex conjugate of the source
impedance.

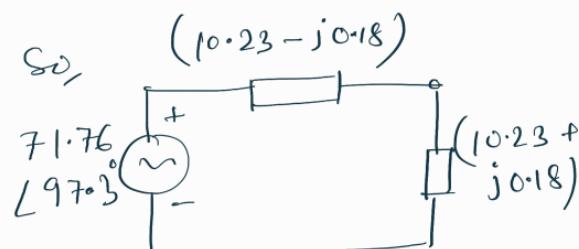
$$\therefore Z_L = (10.23 + j0.18) \Omega$$



$$\begin{aligned}
 P_{max} &= \frac{|V_{TH}|^2}{4R_L} = \frac{|71.76|^2}{4 \times 10.23} \\
 &= \underline{125.84 \text{ W}}
 \end{aligned}$$

Q5(a)

[4 Marks]

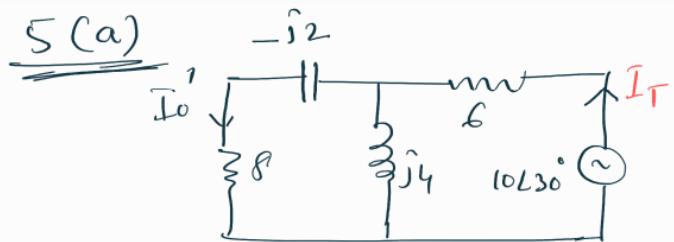

So, when $10\angle 30^\circ$ V is acting alone,

$$Z_T = 6 + \frac{j4(8 - j2)}{j4 + 8 - j2}$$

$$= 8.64 \angle 24.12^\circ \Omega$$


$$I_T = \frac{10\angle 30^\circ}{8.64 \angle 24.12^\circ} = 1.16 \angle 5.88^\circ A$$

By current-division rule,

$$I_0 = 1.16 \angle 5.88 \times \frac{j4}{8 - j2 + j4}$$

$$= 0.56 \angle 81.84^\circ A$$

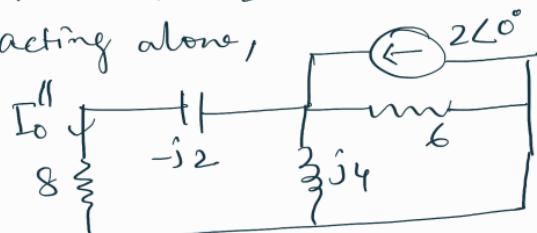
When the $2\angle 0^\circ$ A source is acting alone,



The network can be redrawn as



$\downarrow -j2$

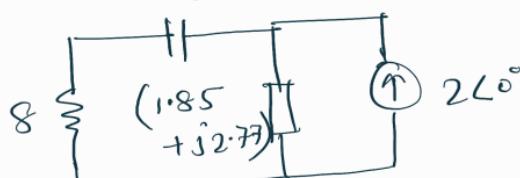


By current division,

$$\underline{I}_o'' = 2 \angle 0^\circ \times \frac{1.85 + j2.77}{1.85 + j2.77 + 8 - j2} \\ = 0.67 \angle 51.83^\circ \text{ A}$$

So, by Superposition Theorem,

$$\underline{I}_o = \underline{I}_o' + \underline{I}_o'' \\ = 0.56 \angle 81.84^\circ + 0.67 \angle 51.83^\circ \\ = 1.19 \angle 65.46^\circ \text{ A}$$

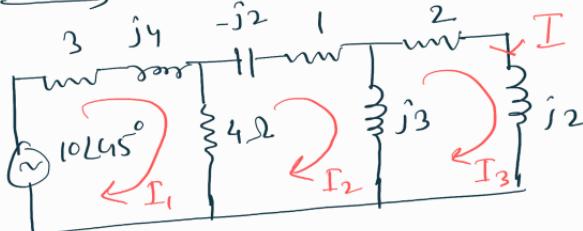5(b)Case TKVL for Mesh I

$$10\angle 45^\circ - (3 + j4)I_1 - 4(I_1 - I_2) = 0$$

$$\Rightarrow (7 + j4)I_1 - 4I_2 = 10\angle 45^\circ \quad (1)$$

KVL for Mesh II

$$-4(I_2 - I_1) - (1 - j2)I_2 - j3(I_2 - I_3) = 0$$

$$\Rightarrow -4I_1 + (5 + j)I_2 - jI_3 = 0 \quad (2)$$

KVL for Mesh III

$$-j3(I_3 - I_2) - 2I_3 - j2I_3 = 0$$


$$\Rightarrow -j3I_2 + (2 + j5)I_3 = 0 \quad (3)$$

we can write (1), (2), (3) as,

$$\begin{bmatrix} 7+j4 & -4 & 0 \\ -4 & 5+j & -j3 \\ 0 & -j3 & 2+j5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10\angle 45^\circ \\ 0 \\ 0 \end{bmatrix}$$

so, by Cramer's rule
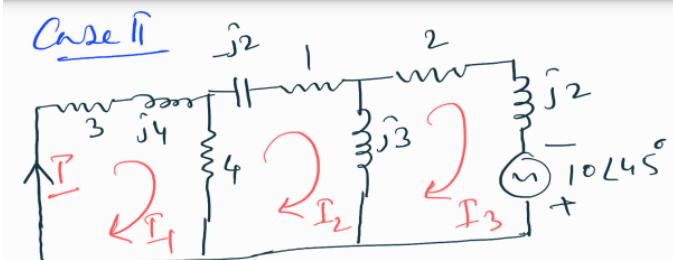
$$I_3 = \frac{\begin{vmatrix} 7+j4 & -4 & 10\angle 45^\circ \\ -4 & 5+j & 0 \\ 0 & -j3 & 0 \end{vmatrix}}{\begin{vmatrix} 7+j4 & -4 & 0 \\ -4 & 5+j & -j3 \\ 0 & -j3 & 2+j5 \end{vmatrix}} = \frac{0.704}{130.72} A \equiv \underline{I}$$



KVL for Mesh I,

$$-(3+j4)I_1 - 4(I_1 - I_2) = 0$$

$$\Rightarrow (7+j4)I_1 - 4I_2 = 0 \quad \textcircled{I}$$

KVL for Mesh II,

$$-j(1-j2)I_2 - (1-j2)I_2 - j3(I_2 - I_3) = 0$$

$$\Rightarrow -4I_1 + (5+j)I_2 - j3I_3 = 0 \quad \textcircled{II}$$

KVL for Mesh III,

$$-j_3(I_3 - I_2) - 2I_3 - j2I_3 + 10∠45° = 0$$

$$-j3I_2 + (2+j5)I_3 = 10∠45° \quad \textcircled{III}$$

Writing eqns \textcircled{I} , \textcircled{II} , \textcircled{III} in matrix form,

$$\begin{bmatrix} 7+j4 & -4 & 0 \\ -4 & 5+j & -j3 \\ 0 & -j3 & 2+j5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 10∠45° \end{bmatrix}$$

So, by Cramer's rule,



$$I_1 = \frac{\begin{vmatrix} 0 & -4 & 0 \\ 0 & 5+j & -j3 \\ 10∠45° & -j3 & 2+j5 \end{vmatrix}}{\begin{vmatrix} 7+j4 & -4 & 0 \\ -4 & 5+j & -j3 \\ 0 & -j3 & 2+j5 \end{vmatrix}}$$

$$= 0.704 \angle 30.72^\circ \text{ A} \equiv \text{I}$$

So, I is same in both the cases.
→ Reciprocity is verified.

Q.6(a)

[1+1+1+2=5 Marks]

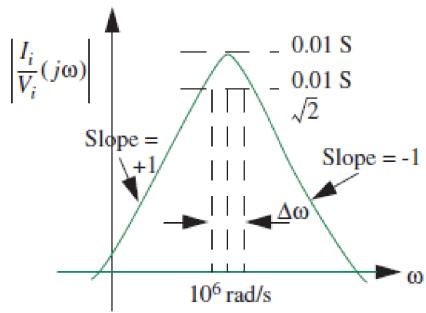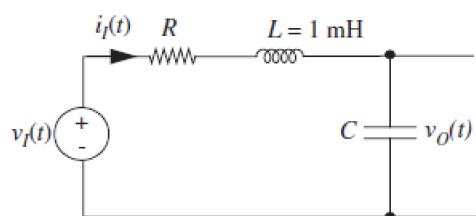

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

a)

$$\omega_0 = 10^6$$

$$C = 10^{-9} F$$

b) at resonance:

$$R = \left\| \frac{V_i}{I_i} \right\| = 100 \Omega$$

c)

$$Q = \frac{\omega_0 L}{R} = 10$$

$$Q = \frac{\omega_0}{\Delta\omega} = 10$$

$$\Delta\omega = 100,000 \frac{\text{rad}}{\text{s}}$$

(d) We have the following equation:

$$\frac{1}{L}v'_I(t) = i'' + \frac{R}{L}i' + \frac{1}{LC}i$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$s = -\frac{R}{2L} \pm j\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} = -5000 \pm j\underbrace{(998, 749)}_{\omega}$$

$$i = A^{st+B}$$


$$v_O = \frac{\int idt}{C} = \frac{A}{Cs}e^{st+B} + D = 1 - e^{-5000t}[A \sin(\omega t) + B \cos(\omega t)]$$

$$v_O(0) = 0 \Rightarrow B = 1$$

$$v'_O(0) = 0 \Rightarrow 5000B - A\omega = 0 \Rightarrow A = 0.005$$


$$v_O(t) = 1 - e^{-5000t}[0.005 \sin(998, 749t) + \cos(998, 749t)]$$

Following is the output plot:

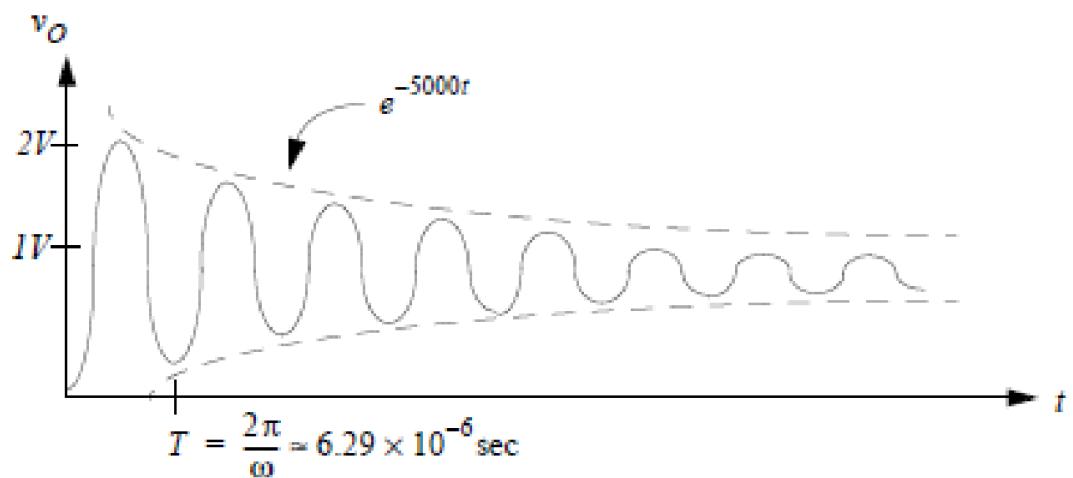

Q6(b)

[5 Marks]

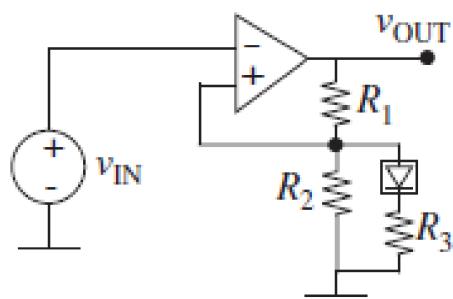

The op amp has a positive feedback. This is an inverting Schmitt trigger circuit.

When the input v_{in} is greater than zero, the output will v_{out} will be negative supply voltage $-V_{cc}$. Thus the diode will be reverse biased.

The potential at the junction of R_1 and R_2 will be $-\frac{R_2}{R_2+R_1}V_{cc}$. The output will switch to positive when v_{in} is less than $-\frac{R_2}{R_2+R_1}V_{cc}$. At this point the output will switch to $+V_{cc}$ and the diode starts conducting.

Thus the voltage at the junction of R_1 and R_2 will be equal to $\frac{\frac{R_2R_3}{R_2+R_3}}{R_1 + \frac{R_2R_3}{R_2+R_3}}V_{cc}$.

$$LTL = -\frac{R_2}{R_2+R_1}V_{cc}$$

$$UTL = \frac{\frac{R_2R_3}{R_2+R_3}}{R_1 + \frac{R_2R_3}{R_2+R_3}}V_{cc}$$

